
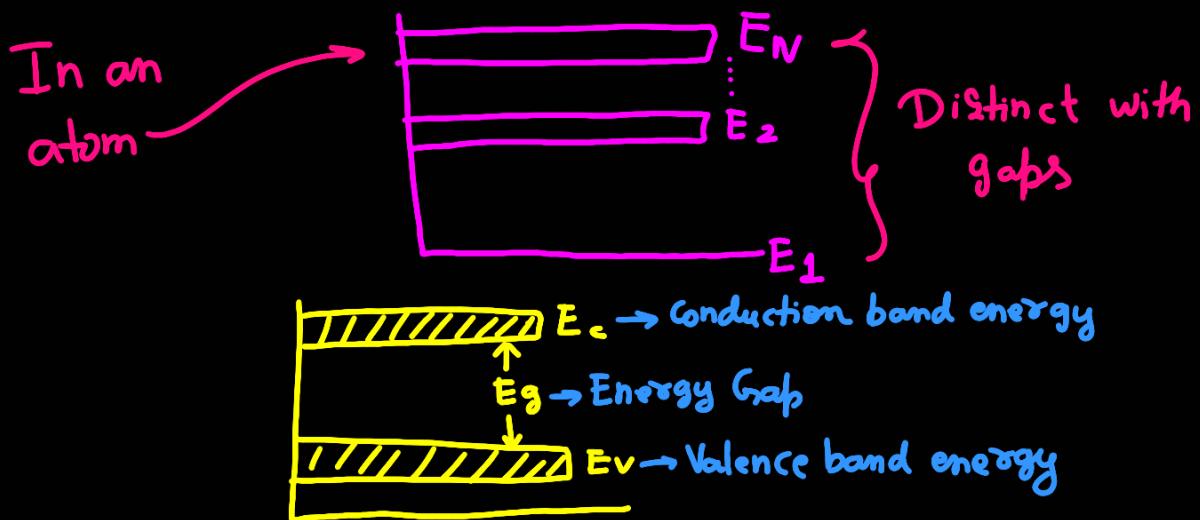


Diode: → It is an electronic device
↳ Easily control of e^- flow

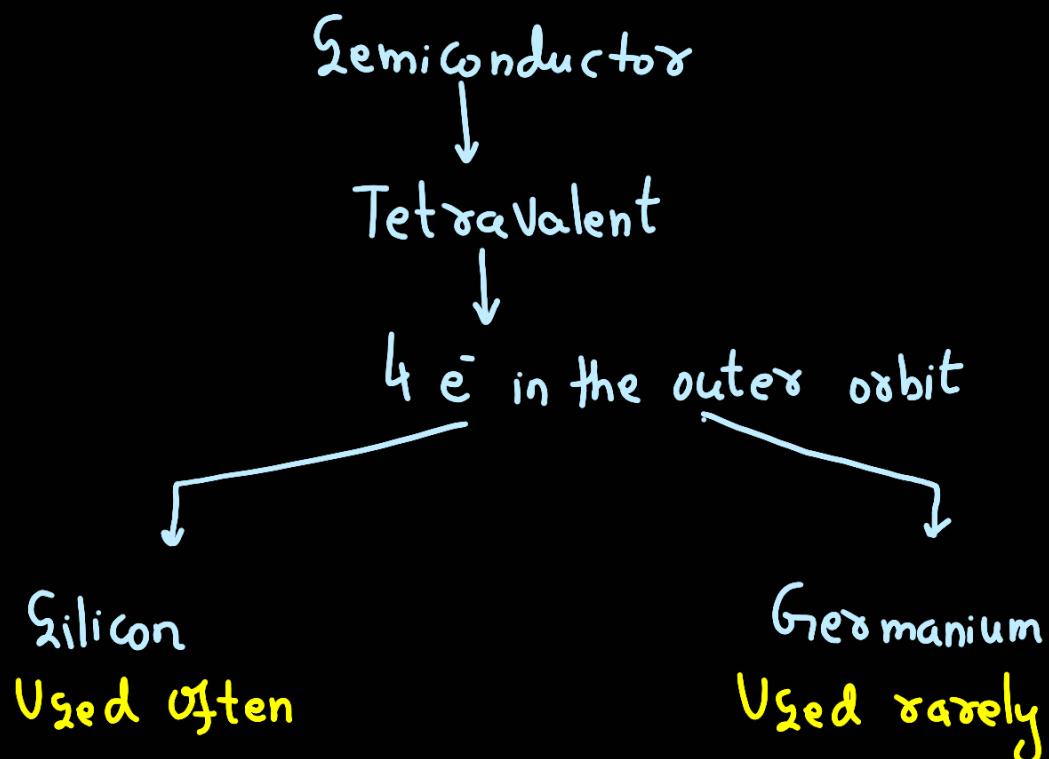
Semiconductor → Neither a conductor nor insulator



Any e^- in E_g will return to the valence band & emit radiation




Energy diagram of Semiconductor

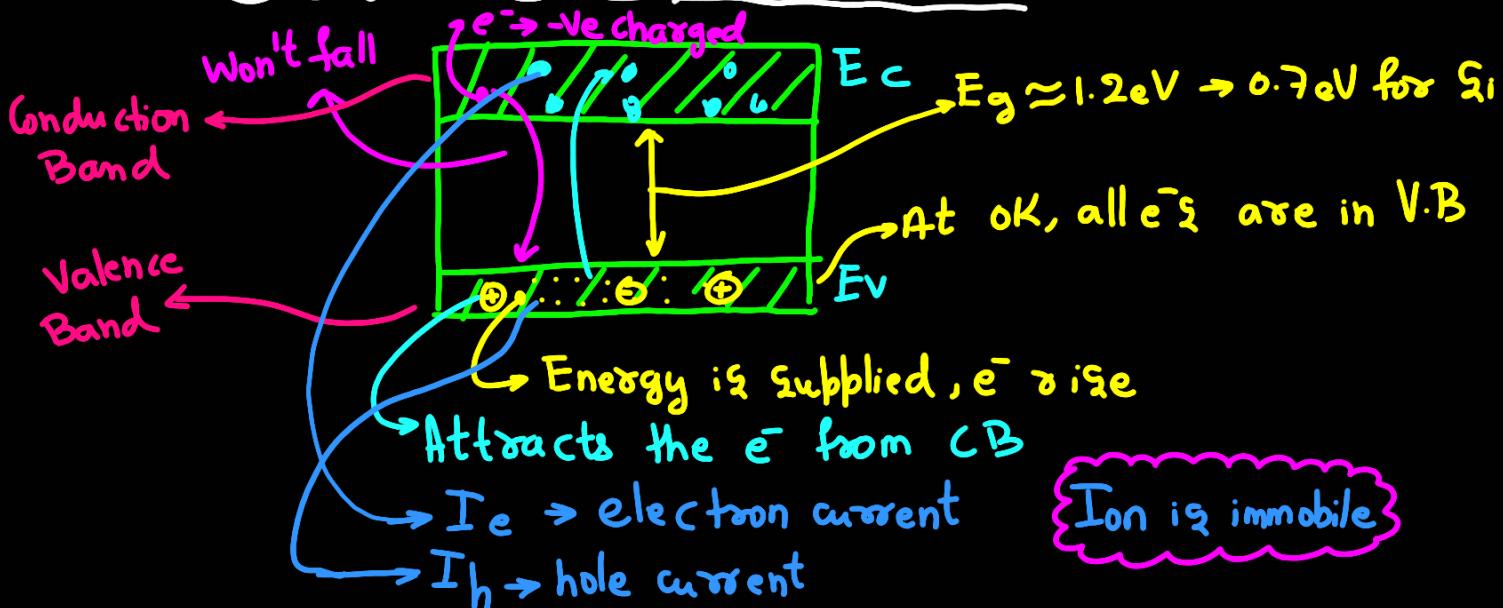


Total Current $\rightarrow I_T \rightarrow I_T = I_e + I_h$


This entire process repeats again

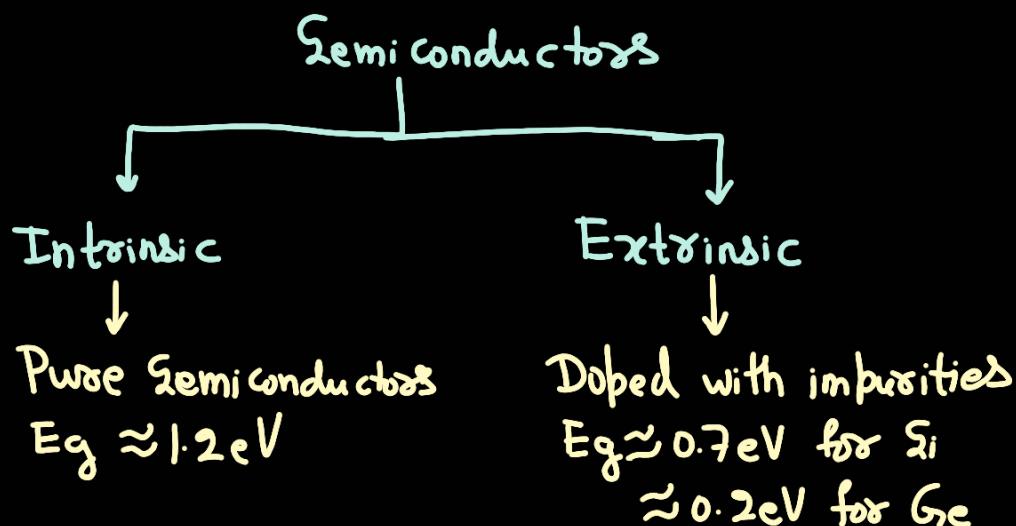

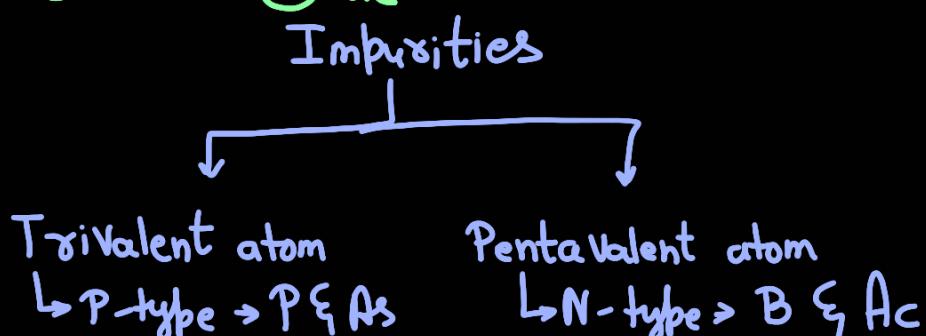Doping :- The method of adding impurities to semiconductors either Si or Ge




N-type Semiconductor :-

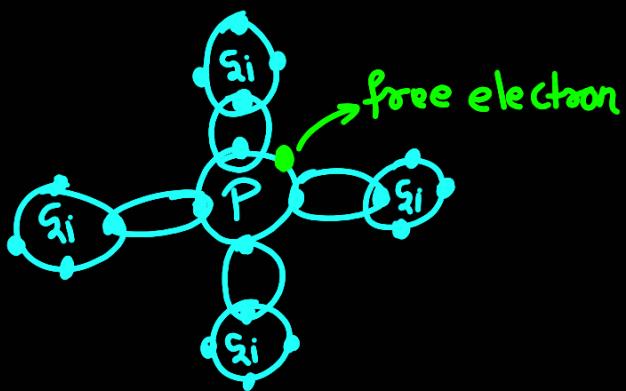


P → donates free e^-
→ Pentavalent donor atom

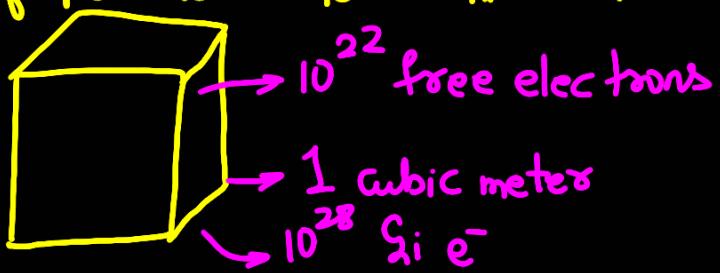Add 1 atom of pentavalent to 1 million atoms of 'Si' atoms




P-type Semiconductor :-

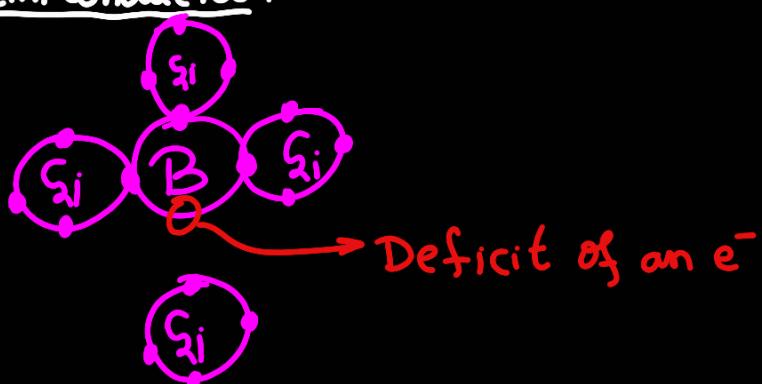

B → Donates hole (has a deficit of e^-)

→ Trivalent acceptor atom

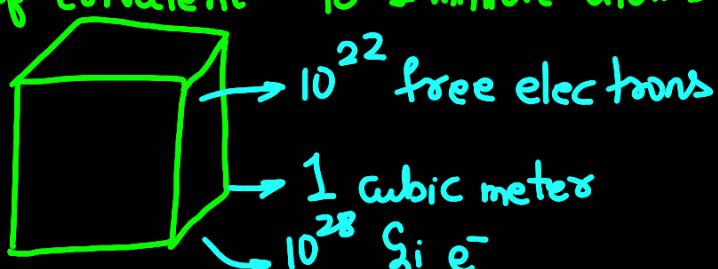Add 1 atom of trivalent to 1 million atoms of 'Si' atoms



Diode :-

→ Electronic Device

→ Semiconductor Diode


↓

2 electrodes



↓

Cathode


Anode

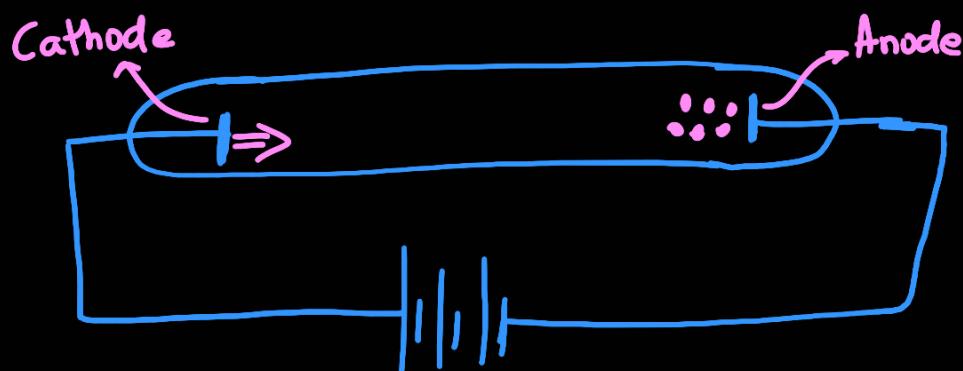

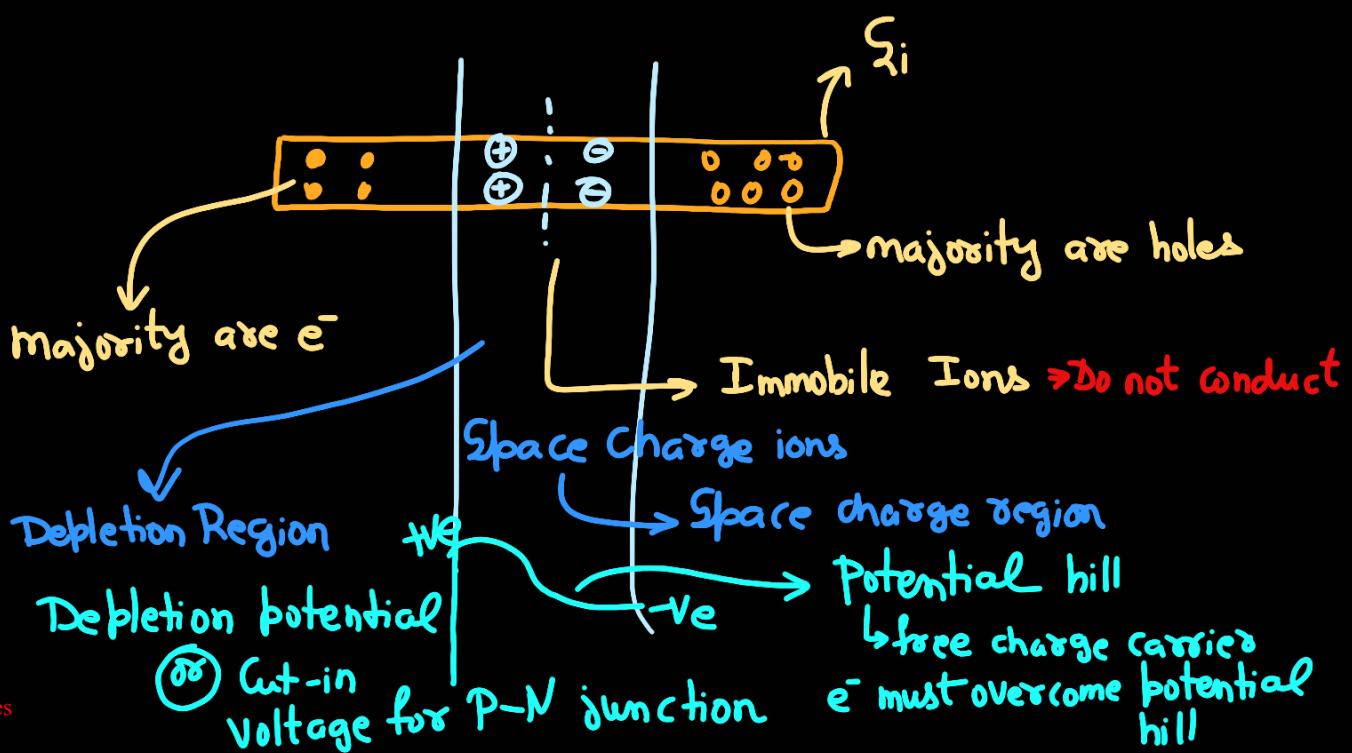
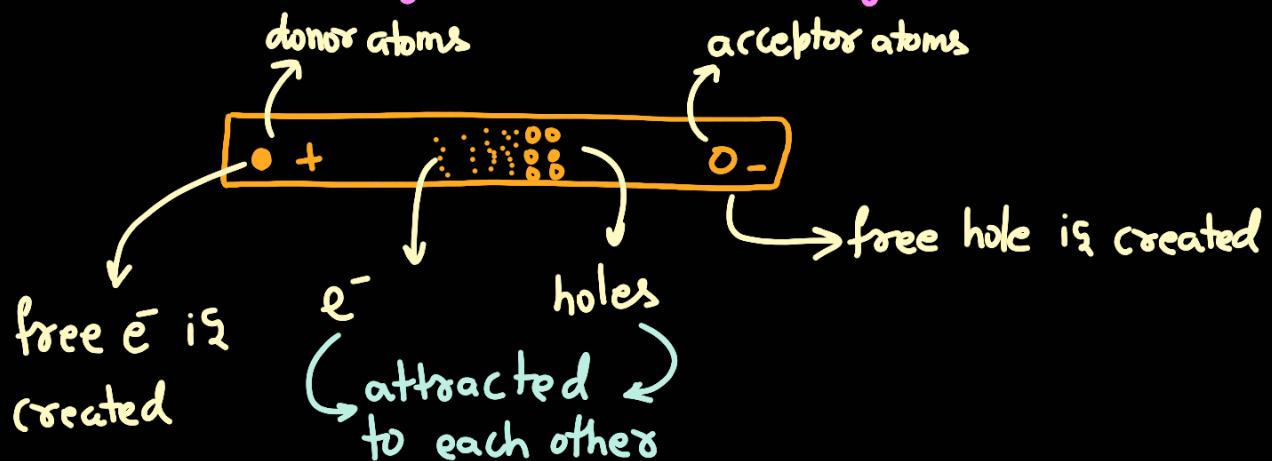
e^- are emitted by cathode & collected by anode



Circuit Symbol for diode:-

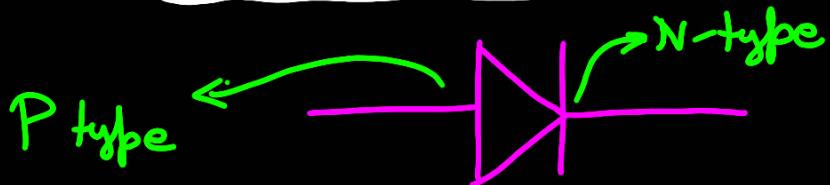



→ Current Direction

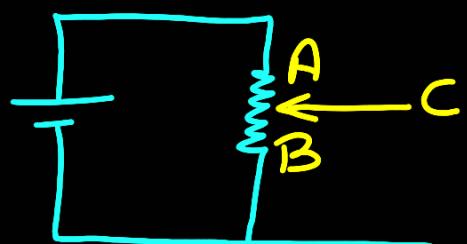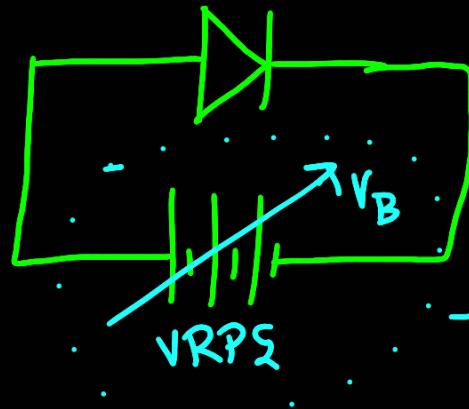


↳ Potentiometers

V-I characteristics of a diode:-

Bias → DC Important
Signal → AC

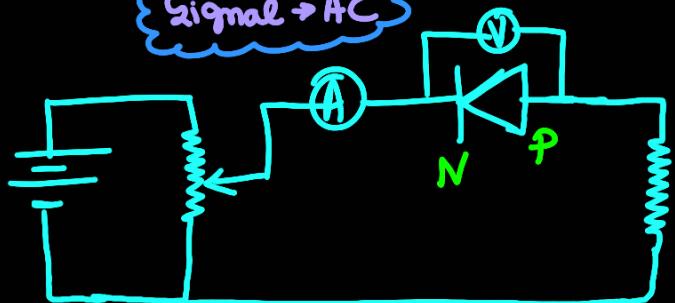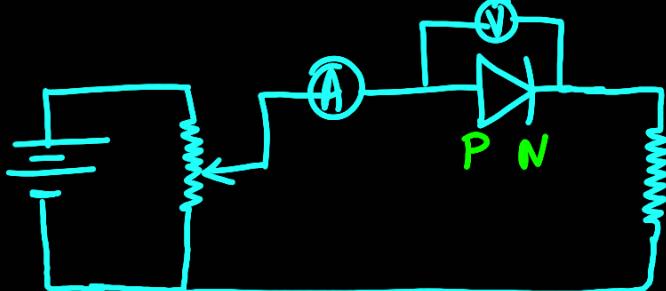

Forward Bias

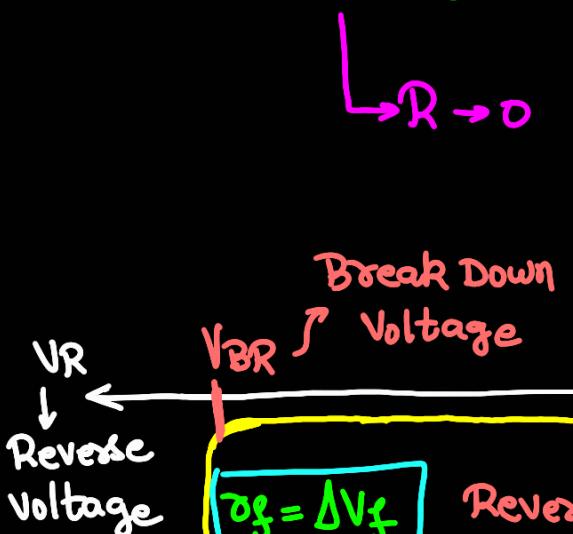

$\rightarrow R \rightarrow 0$

I

$\frac{a_1}{10\Omega}$

100Ω

10Ω

$1A$

$0.1A$

Reverse Bias

$\rightarrow R \rightarrow \infty$

$10A$

$1A$

$0.1A$

10Ω

100Ω

1000Ω

10000Ω

100000Ω

Break Down Voltage V_{BR}

Reverse Voltage V_R

Dynamic Resistance $\frac{\Delta V_f}{\Delta I_f}$

Reverse Saturation Current I_0

AC Current

Dynamic Resistance $\frac{\Delta V_f}{\Delta I_f}$

Reverse Saturation Current I_0


AC Current

Dynamic Resistance $\frac{\Delta V_f}{\Delta I_f}$

Forward Voltage V_f


Static Resistance $R_f = \frac{V_f}{I_f}$

In F.B:-

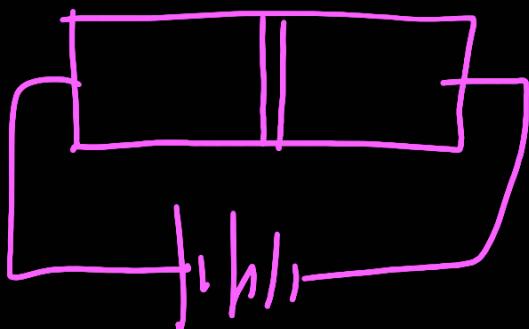

Depletion layer decreases in size

In R.B:-

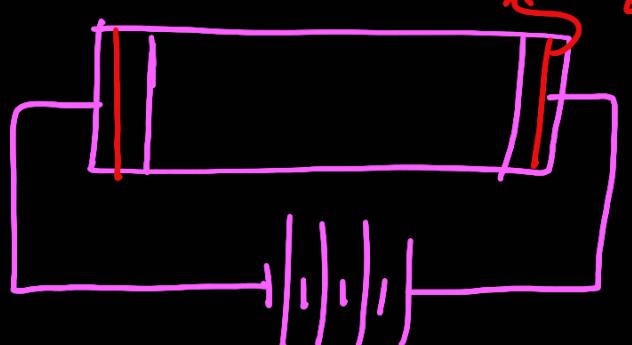

KA-BOOM

Depletion layer increases in size

Current Equation:-

$$I_D = I_0 \left(e^{\frac{V}{\eta V_T}} - 1 \right)$$

I_D → Current through diode

I_0 → Reverse saturation current

V → Applied Voltage

η → Constant $\Rightarrow \xi_i = 2$
 $\xi_e = 1$

V_T → Volt equivalent of temperature

$$V_T = \frac{kT}{qV} \Rightarrow V_T = \frac{T}{11600}$$

→ @ room temp

$$V_T \approx 26mV$$


I_0 doubles for every 10° rise in temp.

T → Temp. in 'K'


AC & DC equivalent circuit:-



DC equivalent ckt when forward biased

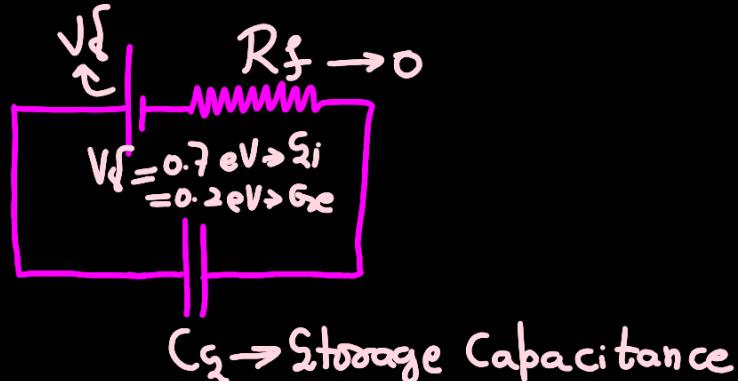

DC equivalent ckt when reverse biased:-

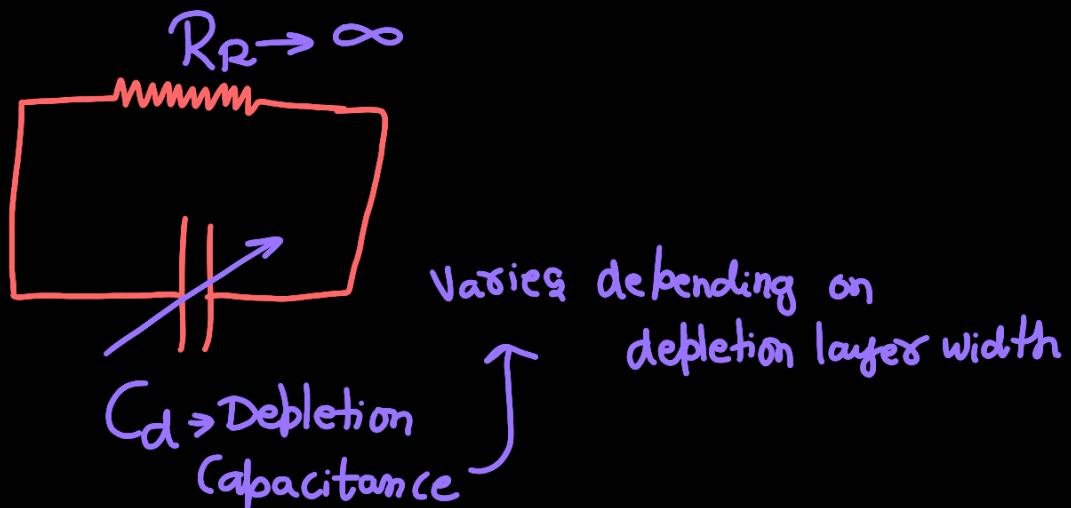


AC equivalent when Forward Biased



AC equivalent when Reverse Biased






Zener Diode :-

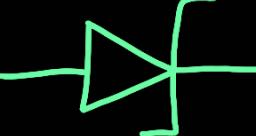→ Ckt symbol :- 
→ P-N junction diode

External voltage $> V_Z$ there flows a large current limited to $I_{Z \text{ max}}$

- ★ Heavily doped
- ★ Current before breakdown is I_0
- ★ Breakdown in ZEN diode at smaller voltage
- ★ Operated in ZEV bias
- ★ Breakdown & maintains constant value called Zener voltage

} Characteristics of Zener Diode

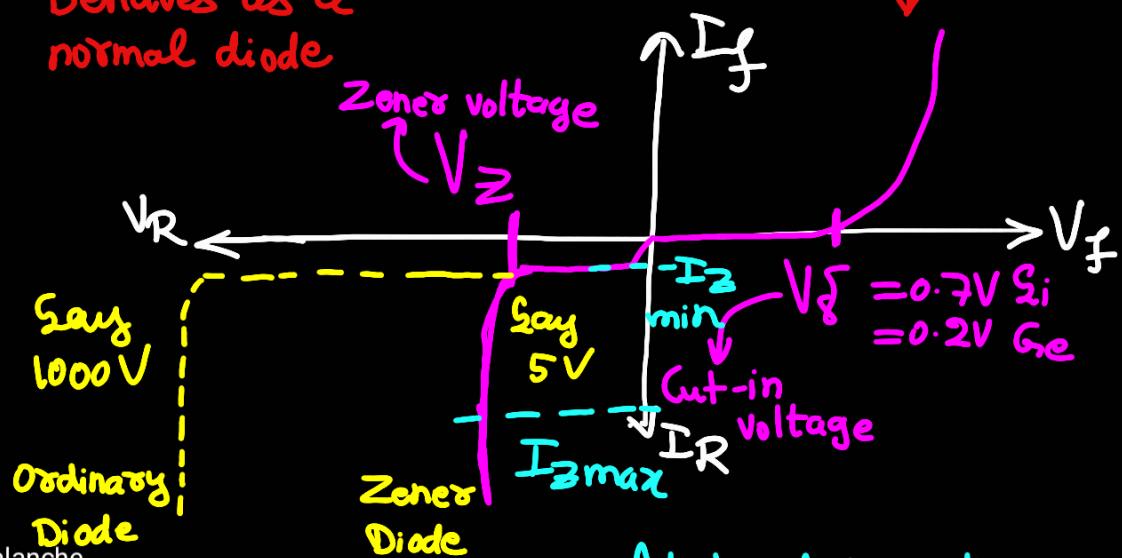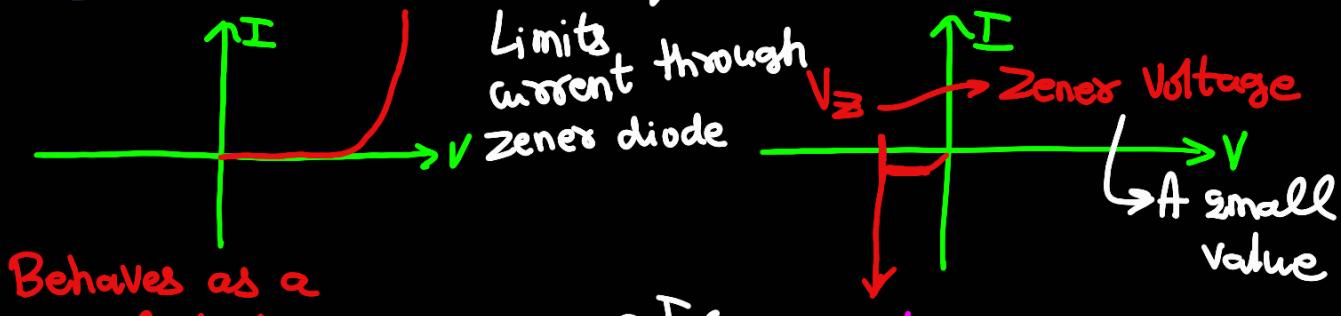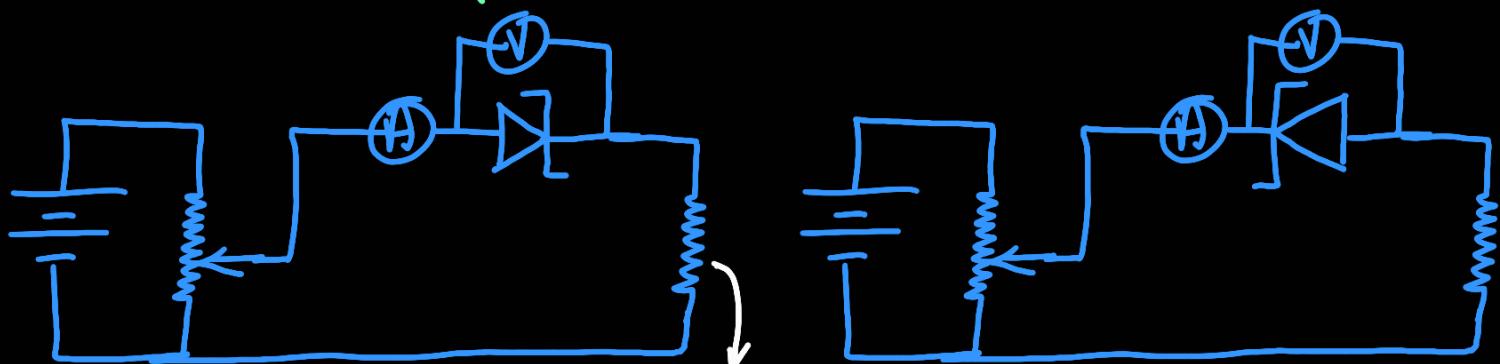

Avalanche breakdown is the breakdown that occurs in normal diode & that happens because of physical effect where electrons impact on the atoms

Zener breakdown is the breakdown that occurs in zener diode & that happens because of quantum effect

At breakdown, there is heavy power dissipation. This causes the diode to get damaged. Thus, there is a Zener Operating Region

A resistor in series with the Zener diode, limits current to $I_{Z(\text{max})}$

$$P_Z = V_Z I_{Z \text{ max}}$$


$$\gamma_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

Tunnel diode :-

- Ckt Symbol :- 
- Special diode
- Heavily doped


7. On further increment of temperature the conduction band (of N-Type) now goes above the valence band (of P-Type).
8. The flow of electrons reverses and now moves from E_V to E_C . (From lower potential to higher potential)
9. Now the resistance decreases as the electrons now move from valence band to conduction band. Since now at conduction band electrons keeps on increasing conductivity also increases, *Upto a certain point*.
10. Later tunnel diode breakdown and burns out on further increment of temp

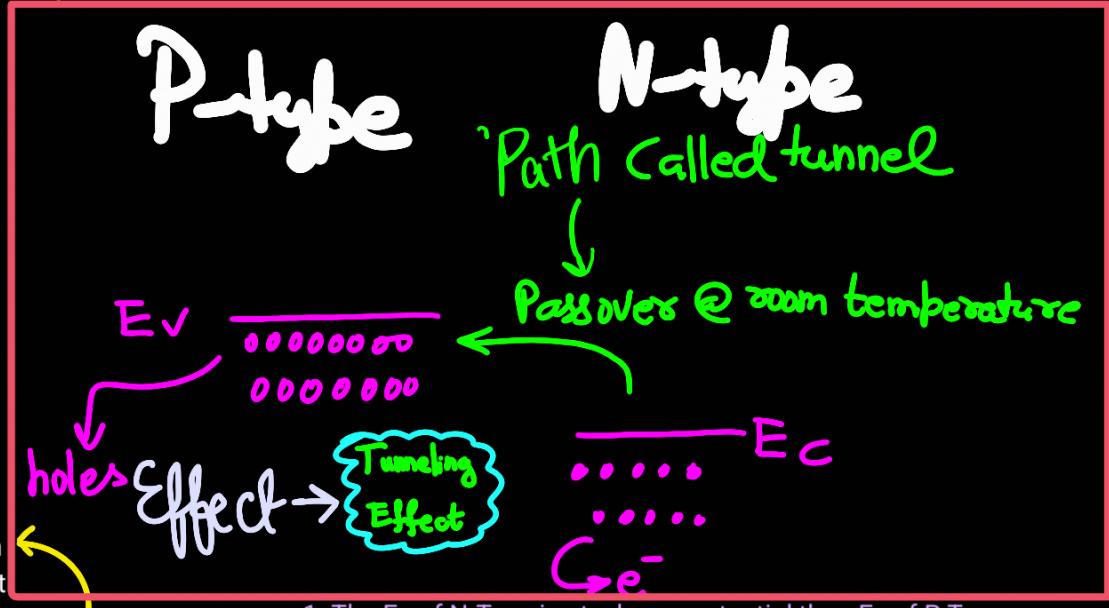6. At a point both conducting & valence band E_C & E_V will be at the same level.
At that point, Current is highest called as tunneling current.



1. The E_C of N-Type is at a lower potential than E_V of P Type.
2. On increasing temperature the electrons start jumping from E_C to E_V ($N \rightarrow P$ type), the path followed is called as tunnel.
3. More temperature Inc. More electrons jump
4. When the electrons jump, the potential of E_C also increases.
5. Resistance keeps on inc. As no. Of electrons in conduction band reduce as they jump into valence band

★ V-I characteristics of Tunnel Diode :-

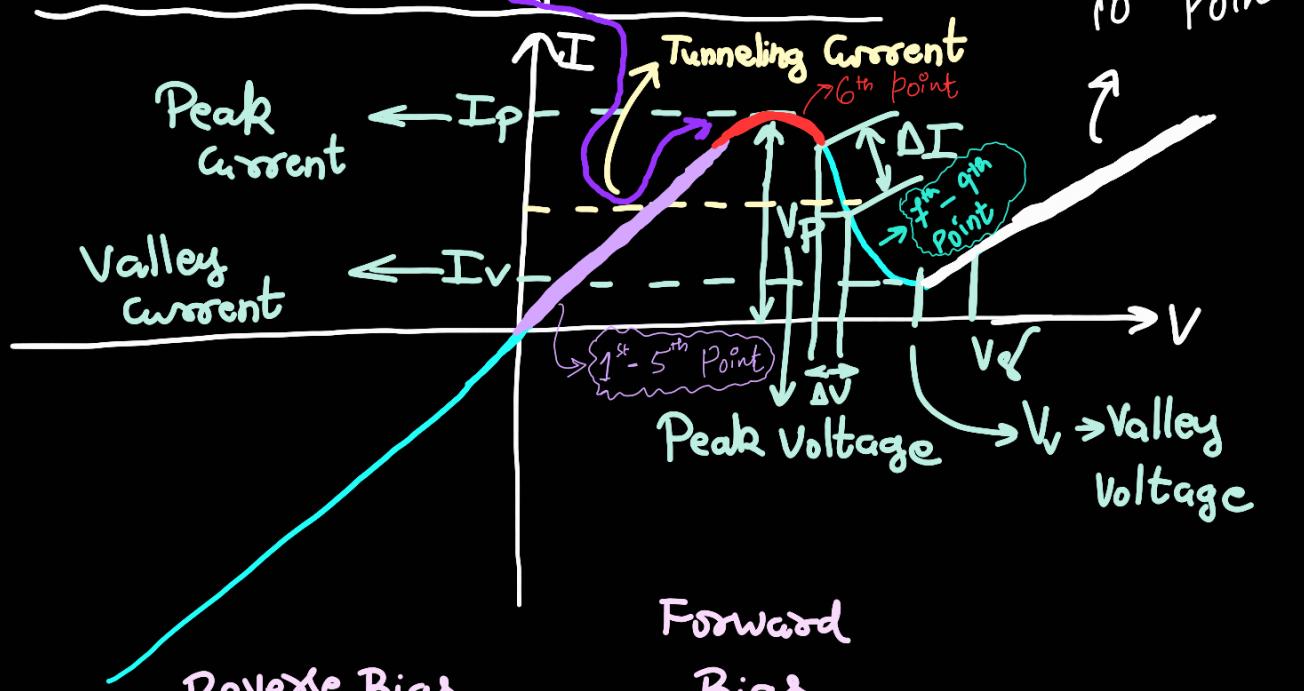

Ordinary diode when $V_f > V_f$

★ $V_f < V_f \rightarrow$ Current rises (Tunneling) \rightarrow for $V_f < V_f$

★ $V_p < V_f < V_f \rightarrow$ Current decreases

Types of Breakdown:-

Zener Breakdown

→ Covalent bonds of depletion layer break due to high electric field of very high reverse bias voltage

→ P-N junction having "high doping" & thin depletion layer

Avalanche Breakdown

Covalent bonds of depletion layer are broken by collision of "minorities" which acquire high K.E from elec field of very very high reverse bias voltage

→ P-N junction having "low doping" & thick depletion layers


Rectifiers:-

→ Converts AC to DC

Half-wave rectifier

$\text{AC} \rightarrow \text{DC}$


Full wave rectifier

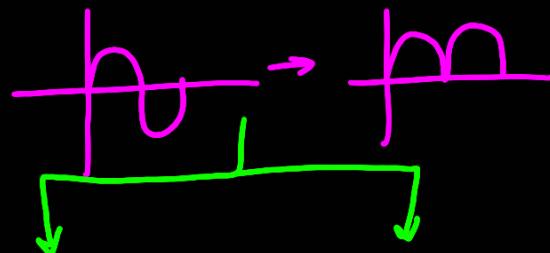


Center tapped FWR

Bridge FWR

Half-wave Rectifier

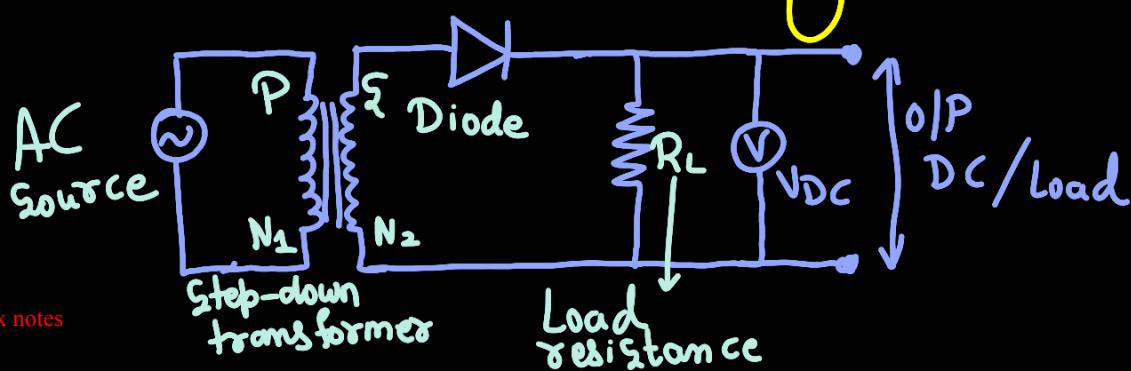

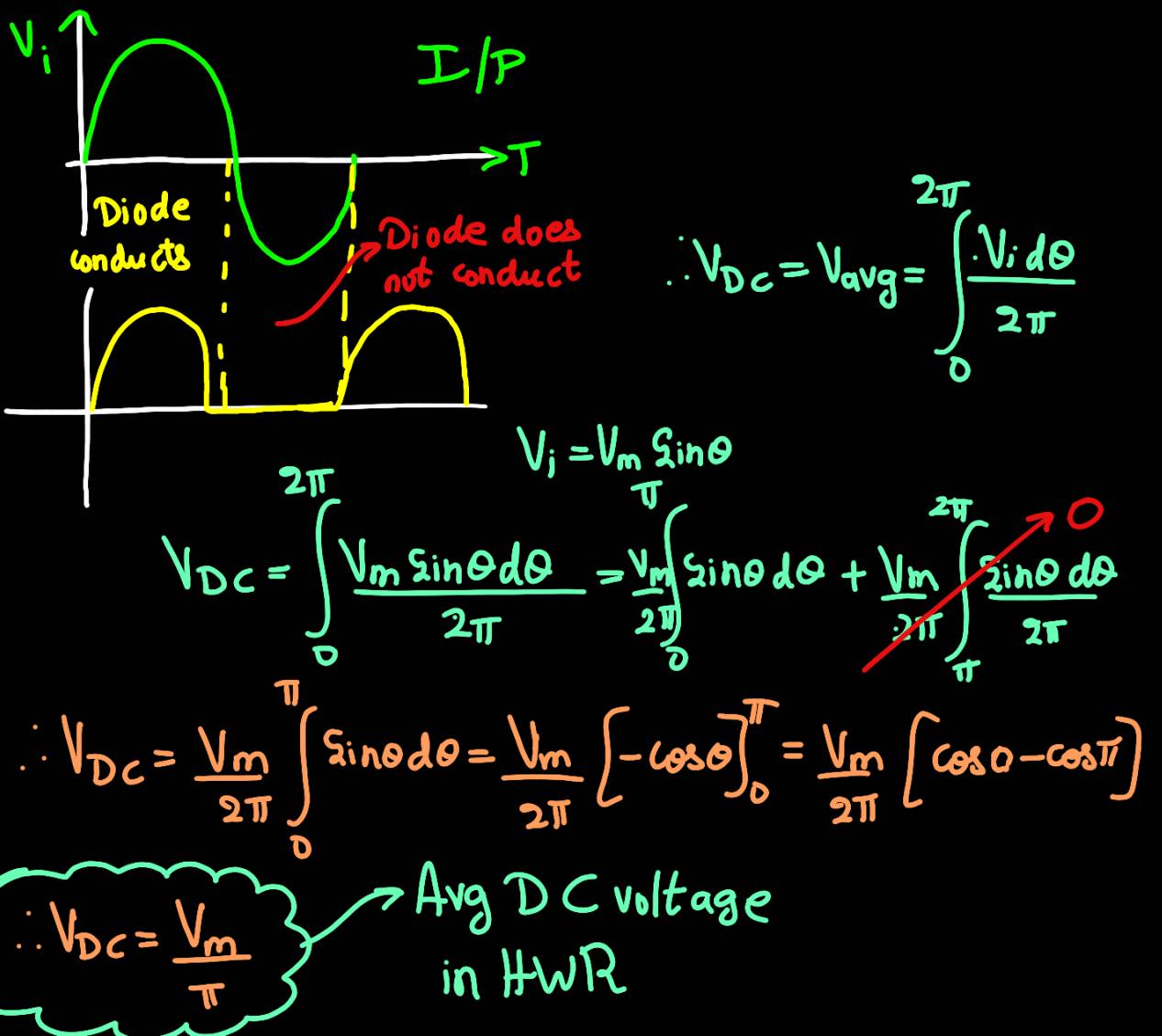

Ripple Factor :-

$$\delta = \frac{\text{AC Component}}{\text{DC Component}} \rightarrow V_{rms}(\text{o/p}) = ??$$

$$V_{DC} = \frac{V_m}{\pi}$$

→ Measures the quality of DC current converted

$$\therefore V_{rms} = \sqrt{\int_0^{2\pi} \frac{(V_i)^2 d\theta}{2\pi}} = \sqrt{\int_0^{\pi} \frac{(V_m \sin \theta)^2 d\theta}{2\pi} + \int_{\pi}^{2\pi} \frac{(V_m \sin \theta)^2 d\theta}{2\pi}}$$

Diode not conducting

$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} \sin^2 \theta d\theta} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2\theta}{2} d\theta}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \cdot \frac{1}{2} [\pi - 0]}$$

$\therefore V_{rms} = \frac{V_m}{2}$ At the O/P of the HWR

After Substitution :-

$$\delta = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1} = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1}$$

Putting $V_{rms} = \frac{V_m}{2}$; $V_{DC} = \frac{V_m}{\pi}$, we get,

$\delta = 1.21$ Constant for HWR

Implies AC component is 121% more than DC component

* Efficiency:-


$$\% \eta = \frac{\text{O/P Power} \times 100\%}{\text{I/P Power}} = \frac{I_{DC}^2 R_L \times 100\%}{I_{rms}^2 R_L}$$

After putting I_{rms} & I_{DC} values, we get

$\% \eta = 40.5\%$ Due to high ripple

Full-Wave Rectifiers:-

Center-tapped FWR:-

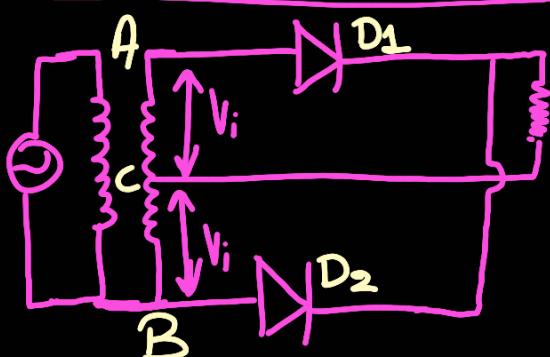

During +ve half cycle

Point A > most +ve, B > -ve

C is less +ve than A (-ve)

D1 conducts

D2 OFF

During -ve half cycle


Point B > most +ve, A > -ve

C is less +ve than B (-ve)

D2 conducts

D1 OFF

Bridge Full Wave Rectifier:-

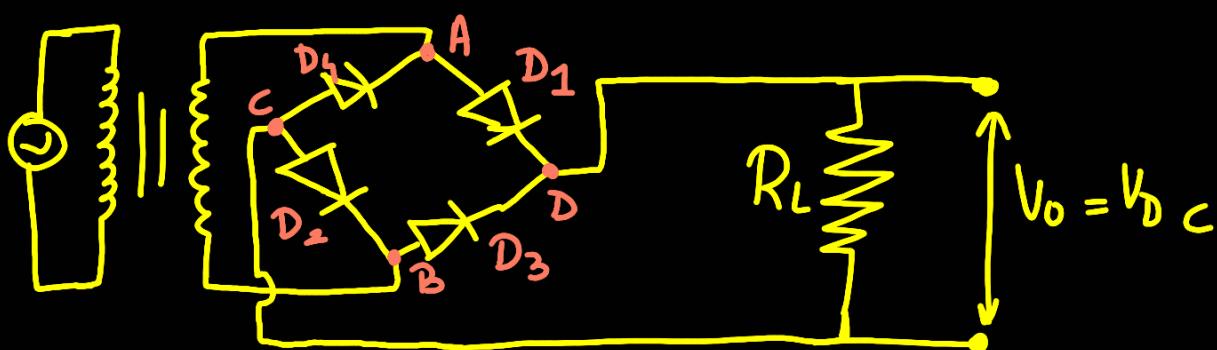

During +ve half cycle

Point A is most +ve & B is most -ve

$\therefore D_1 \& D_2 \rightarrow F.B \rightarrow ON \rightarrow$ Conduct

$D_3 \& D_4 \rightarrow R.B \rightarrow OFF \rightarrow$ Do not conduct

Current flows from D1, flows through RL from point D to C




Current flow direction

During -ve half cycle

Point B \rightarrow most +ve; A \rightarrow most -ve

$D_3 \& D_4 \rightarrow F.B \rightarrow ON \rightarrow$ conduct

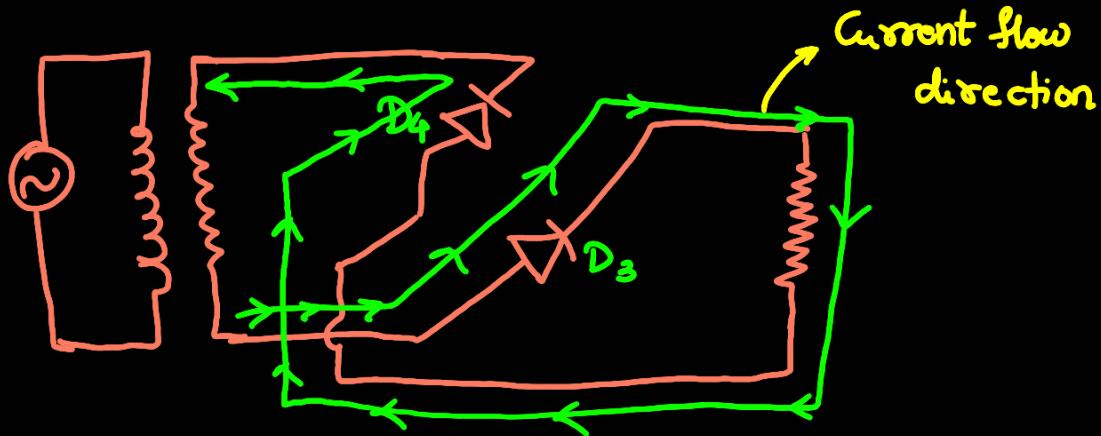$D_1 \& D_2 \rightarrow R.B \rightarrow OFF \rightarrow$ Do not conduct



V_{DC} , V_{rms} & g of FWR (Same for both) :-

Draw
IP o/P
waveforms

$$V_{DC} = \int_0^{2\pi} \frac{V_m \sin \theta d\theta}{2\pi} = \int_0^{\pi} \frac{V_m \sin \theta d\theta}{2\pi} + \int_{\pi}^{2\pi} \frac{V_m \sin \theta d\theta}{2\pi}$$

$$= 2 \int_0^{\pi} \frac{V_m \sin \theta d\theta}{2\pi} = \frac{V_m}{\pi} \left[-\cos \theta \right]_0^{\pi} = \frac{V_m}{\pi} (-(-1) + 1)$$

$\therefore V_{DC} = \frac{2V_m}{\pi}$

$$V_{rms} = \sqrt{\int_0^{2\pi} \frac{(V_i)^2 d\theta}{2\pi}} = \sqrt{\int_0^{2\pi} \frac{(V_m \sin \theta)^2 d\theta}{2\pi}}$$

$$= 2 \int_0^T V_m^2 \left(\frac{1 - \cos 2\theta}{2} \right) d\theta$$

$\Rightarrow V_{rms} = \frac{V_m}{\sqrt{2}}$

Ripple factor :-

$$\xi = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1} = \sqrt{\left(\frac{V_m}{\sqrt{2}} \times \frac{\pi}{2V_m}\right)^2 - 1}$$


$$= \sqrt{\frac{\pi^2}{8} - 1}$$

$\Rightarrow V_{rms} = 0.483$

AC component is 48% more than DC component

$$\text{Efficiency} : \% \eta = \frac{\text{Output Power}}{\text{Input Power}} \times 100 = \frac{I_{DC}^2 R_L}{I_{rms}^2 R_L} \times 100$$


$\therefore \% \eta = 81.05\%$

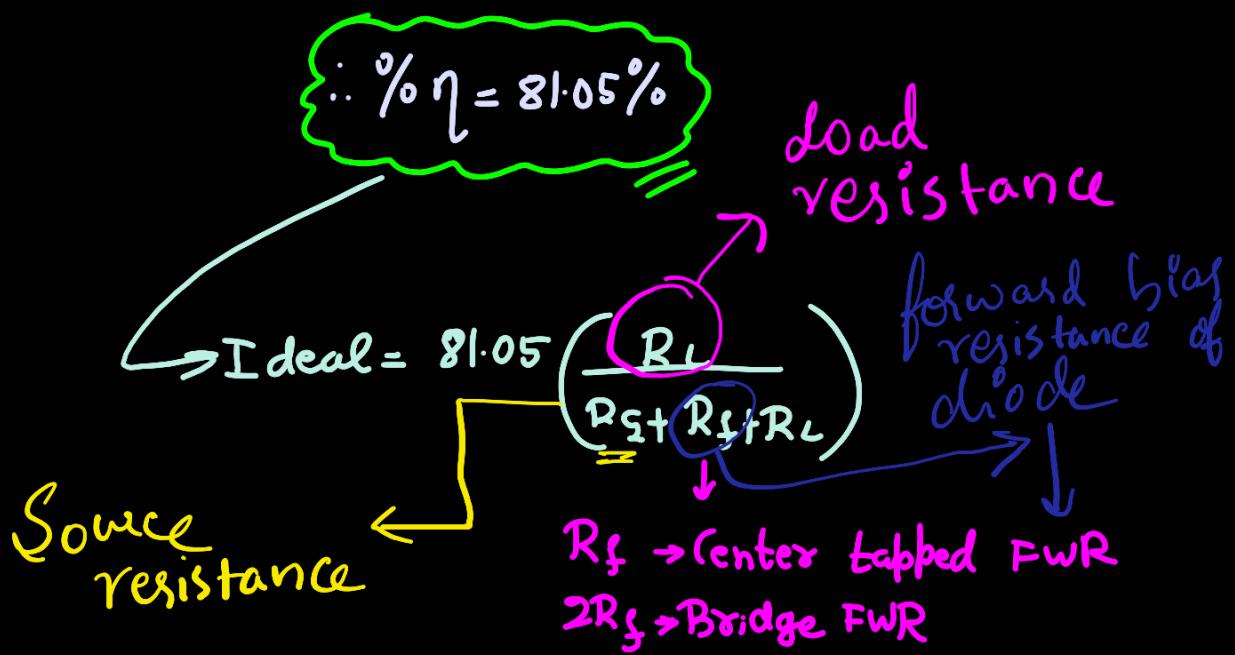

C-filter :-




Capacitor

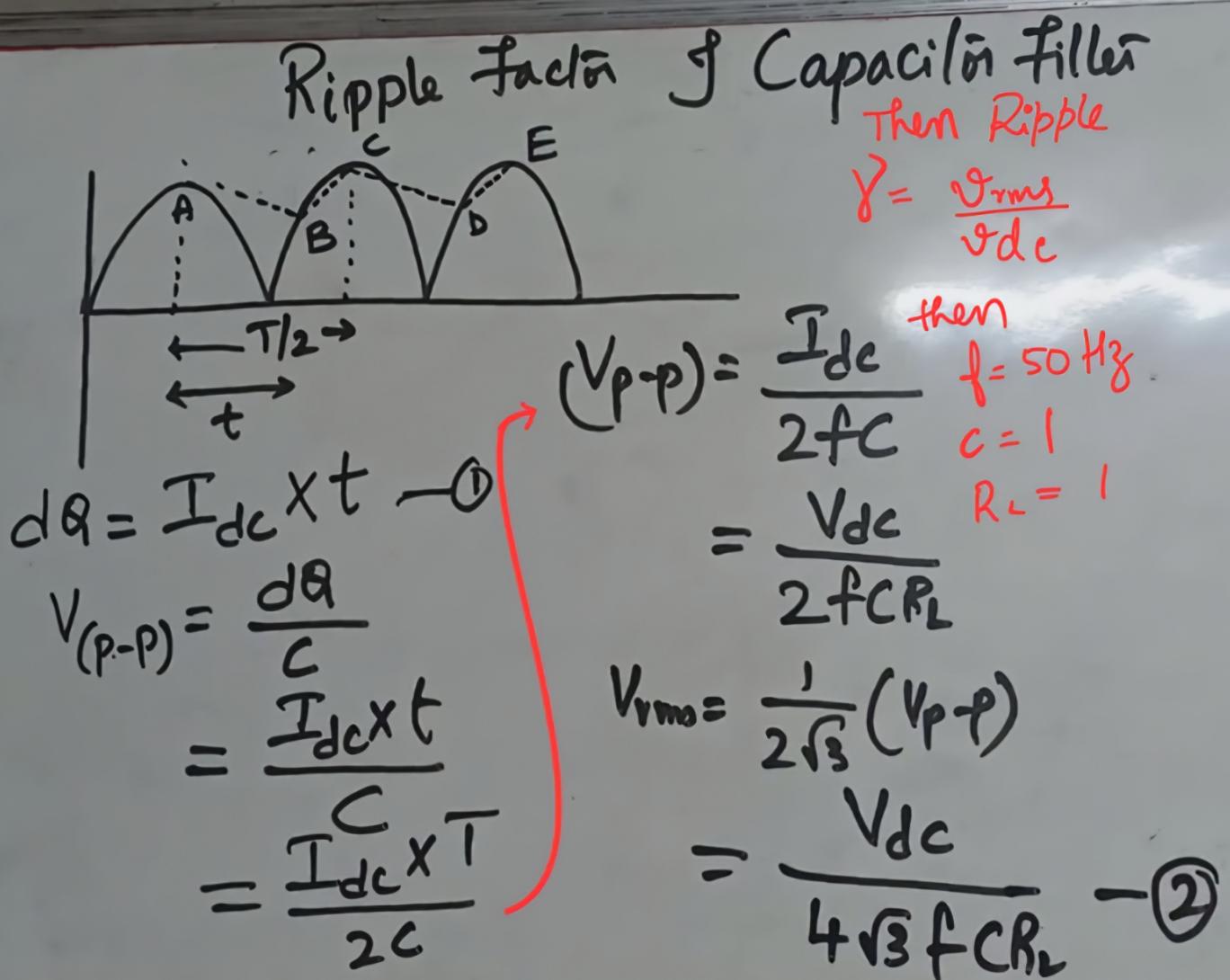



C-filter :-

$$\tau = RC \quad \text{Time Constant}$$

Capacitor

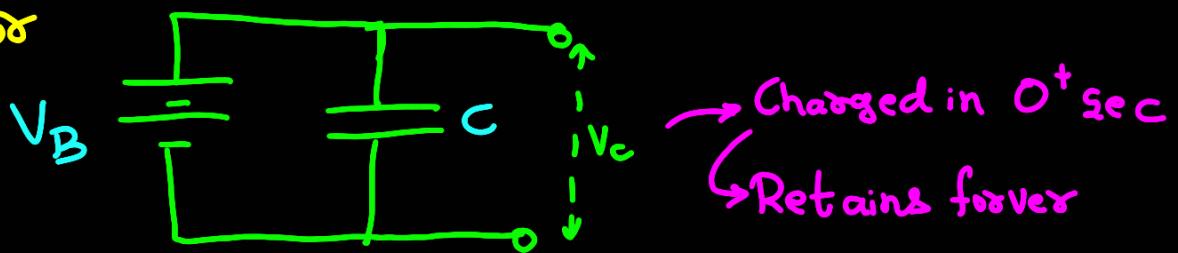


Capacitor charges until $V_C = V_B$

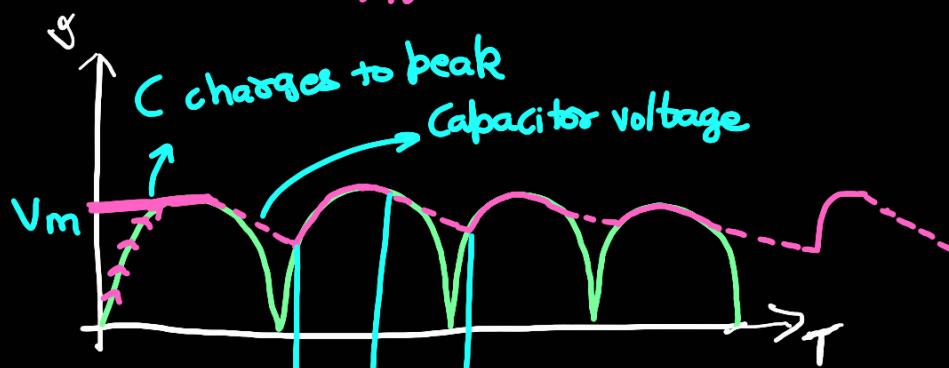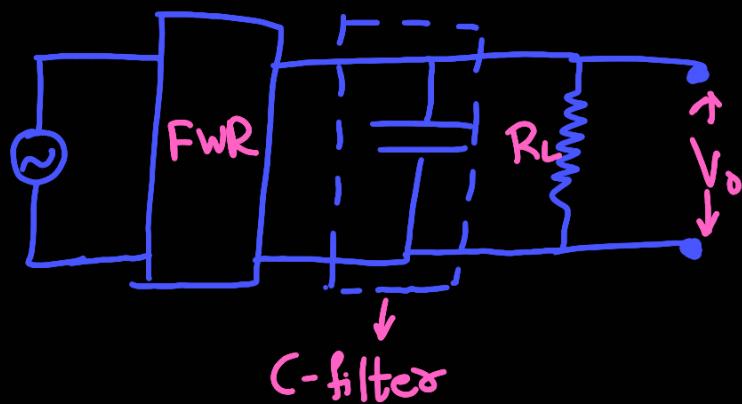

Charging time

Discharging time

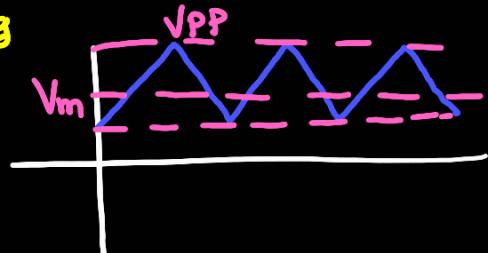

$$V_{\delta \text{ rms}} = \frac{V_m}{\sqrt{3}} ; V_m = \frac{V_{pp}}{2}$$

$$V_{\delta \text{ rms}} = \frac{V_{pp}}{2\sqrt{3}}$$

$$I_{DC} \times \frac{1}{2f} = V_{pp} \times C$$

$$V_{PP} = \frac{I_{DC}}{2fC} ; V_{rms} = \frac{I_{DC}}{2fC} \times \frac{1}{2\sqrt{3}}$$

$$V_{rms} = \frac{V_{DC}}{4\sqrt{3}fCR_L}$$

$$\text{Ripple factor} = \frac{V_{rms}}{V_{DC}} = \frac{V_{DC}}{4\sqrt{3}fCR_L} \times \frac{1}{V_{DC}}$$

$$\delta = \frac{1}{4\sqrt{3}fCR_L}$$

$C \ll R_L \rightarrow \text{Unity}$
 $f = 50 \text{ Hz}$

$\therefore \delta = 0.00288$

Numericals:-

Q) Consider a diode with $I_0 = 0.5 \text{ mA}$. Determine diode current (forward) at room temp

When the diode is subjected to a temp of 373 K, find reverse saturation current of same forward current.

$$\text{Sol}^-: I_D = I_0 \left(e^{\frac{V}{2kT}} - 1 \right)$$

$$\text{(case i)}^-: @ \text{room temp}; V_T = \frac{I}{11600} = \frac{273 + 27}{11600}$$

$$\therefore V_T = 26 \text{ mV}$$

$V_D = 0.7 \text{ V} \rightarrow \text{Diode is assumed to be made of Si}$
 $\Rightarrow \eta = 2$

$$I_D = 0.5 \left(e^{\frac{0.7}{2 \times 26 \times 10^{-3}}} - 1 \right) \times 10^{-3}$$

$$\Rightarrow I_D = 350.946 \text{ mA}$$

$$\text{Case ii:- } V_T = \frac{373}{11600} = 32 \text{ mV}$$

$$I_D = I_0 \left(e^{\frac{V}{V_T}} - 1 \right) \Rightarrow 350.946 = I_0 \left(e^{\frac{0.7}{2 \times 32 \times 10^{-3}}} - 1 \right)$$

$$\Rightarrow I_0 = \frac{350.946}{56387 - 1} \Rightarrow I_0 = 6.22 \text{ mA}$$

- Q) If voltage to a HWR is 10V AC. Determine
 i) load current ii) RMS current, iii) Ripple factor when
 I) Diode is ideal; II) Diode has forward resistance of 5Ω
 & load resistance of 150Ω

Sol:- (Case I) Diode is ideal

$$\text{i) } V_m = 10\sqrt{2} = 14.14 \text{ V}$$

$$I_m = \frac{V_m}{R_L} = \frac{14.14}{150} = 94 \text{ mA}$$

$$I_{DC} = \frac{I_m}{\pi} = \frac{94 \times 10^{-3}}{\pi} = 29.9 \text{ mA} \approx 30 \text{ mA}$$

$$I_{rms} = \frac{I_m}{2} = \frac{94 \times 10^{-3}}{2} = 47 \text{ mA}$$

$$\zeta = \sqrt{\left(\frac{I_{rms}}{I_{DC}}\right)^2 - 1} = \sqrt{\frac{\pi^2}{4} - 1} = 1.21 \Rightarrow \text{constant for HWR}$$

Case II :-

i) $V_m = 14.14 V$

$$I_m = \frac{14.14}{150+5} = 91 mA$$

$$I_{DC} = \frac{91 \times 10^{-3}}{\pi} = 29 mA$$

$$I_{rms} = \frac{91 \times 10^{-3}}{2} = 45.5 mA$$

$$\gamma = \sqrt{\frac{I^2}{4} - 1} = 1.21$$

Q) Center tapped FWR has 2° voltage $10 \sin 3/4t$ on both halves.
Determine O/P voltage & efficiency when

i) Diode is ideal ; ii) has $R_f = 10 \Omega$ & $R_L = 50 \Omega$

Sol:-

Case i:- $V_m = 10 V$

$$V_{DC} = \frac{2V_m}{\pi} = \frac{2 \times 10}{\pi} = 6.366 V$$

$$\% \eta = \frac{I_{DC}^2 \times R_L}{I_{rms}^2 R_L} \times 100\% = \left(\frac{2I_m}{\pi} \right)^2 \times \left(\frac{\sqrt{2}}{I_m} \right)^2 = 81.05\%$$

$$\text{Case ii:- } V_{DC} = \frac{2V_m}{\pi} \times \frac{R_L}{R_f + R_L} = \frac{2 \times 10}{\pi} \times \frac{50}{10 + 50}$$


$$V_{DC} = 5.3 V$$

$$\% \eta = 81.05 \times \frac{50}{50 + 10} = 67.54\%$$

Zener Regulator:-

↳ Maintains a constant voltage (O/P) for any variation in the input voltage or variation in the load resistance

* Simple Zener Regulator:-

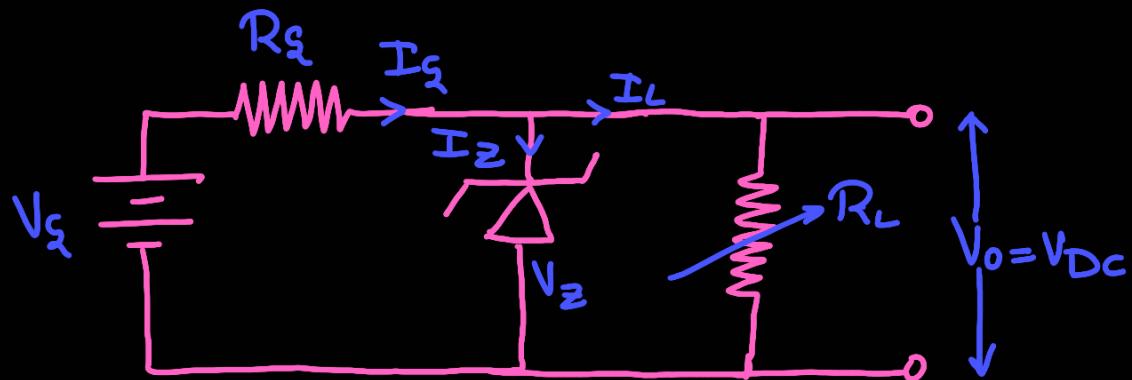

Line Regulation

When I/P voltage varies but R_L is constant

$$\%R_{line} = \frac{\Delta V_O}{\Delta V_S} \times 100\%$$

Load regulation

When R_L varies but I/P voltage is constant

$$\%R_{L(min)} = \frac{V_{S(min)} - V_Z}{I_{Z(min)} + I_{L(max)}} \times 100\%$$

V_S → Source voltage

V_Z → Voltage across Zener diode

I_Z → Current through Zener diode

I_L → Current through load

R_L → Load resistance

R_S → Source resistance


$$\%R_{L(max)} = \frac{V_{S(max)} - V_Z}{I_{Z(max)} + I_{L(min)}} \times 100\%$$

No load voltage
 $\%R_L = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$

Full load voltage

Block diagram of Battery charger

Battery Charger:-

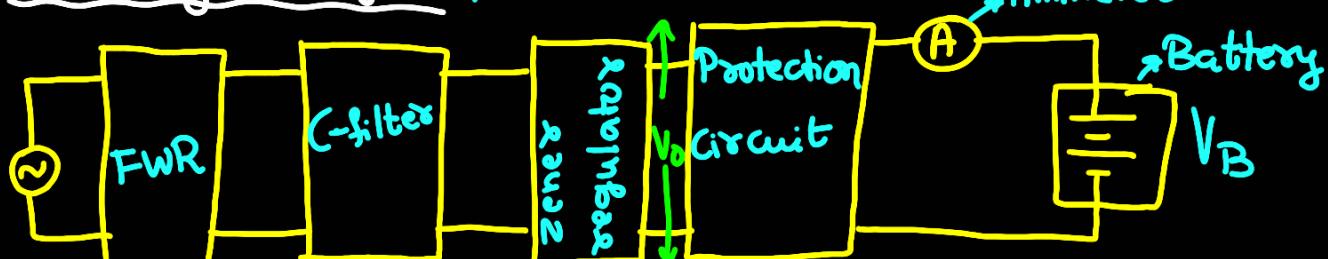

★ The Protection circuit protects the battery from overcharging

★ Ammeter is used to monitor the current through the battery

★ O/P voltage V_o must be greater than the battery voltage for charging to occur.

$$V_o > V_B$$

Clippers:-

★ Used to clip part of the I/P wave form




★ Clippers are used in wave shaping circuits

★ The clippers can be either positive clipper or negative clipper.




★ The +ve or -ve clipper can be either series or shunt

Clippers & Transfer Characteristics:-



Series -ve
Clipper

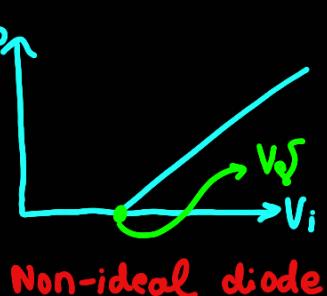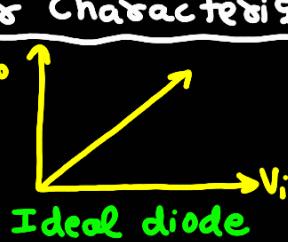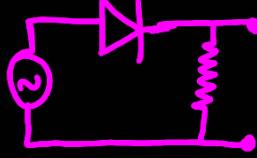

Series +ve
Clipper

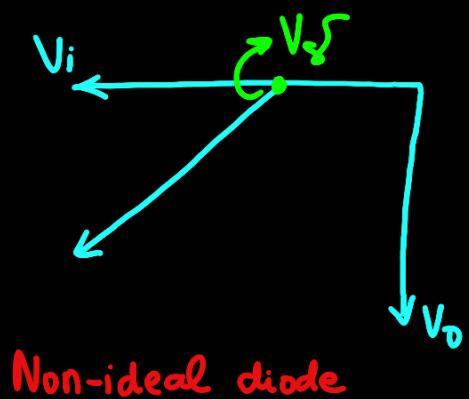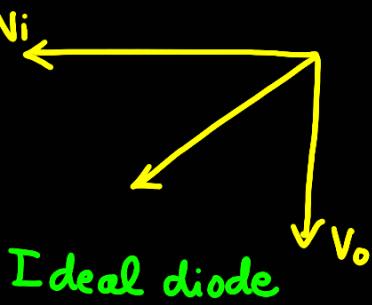
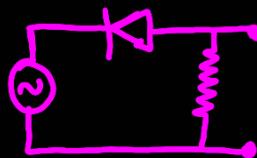


UU O/P

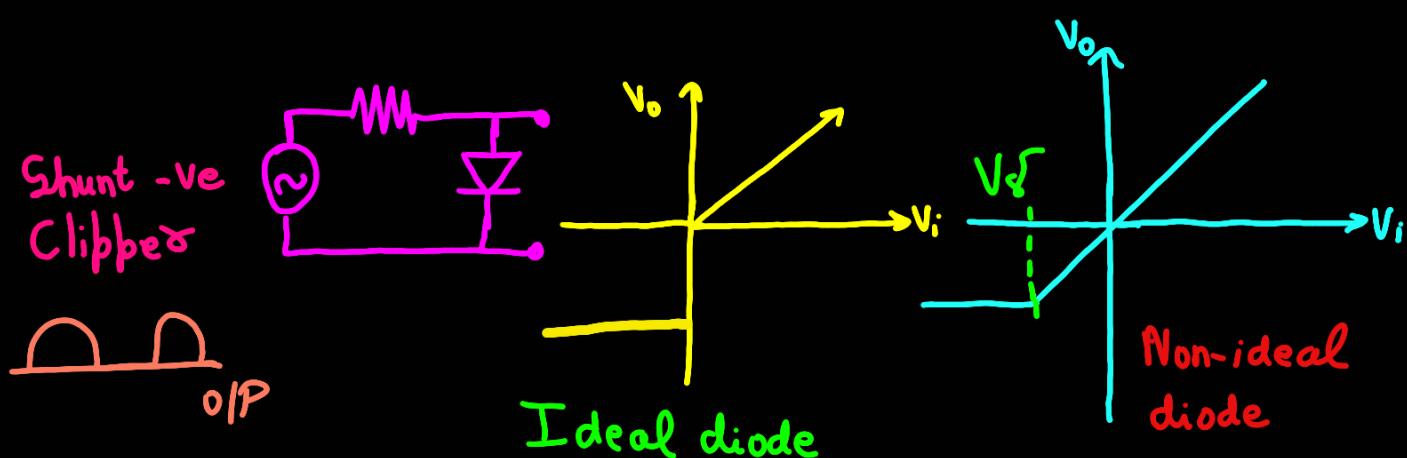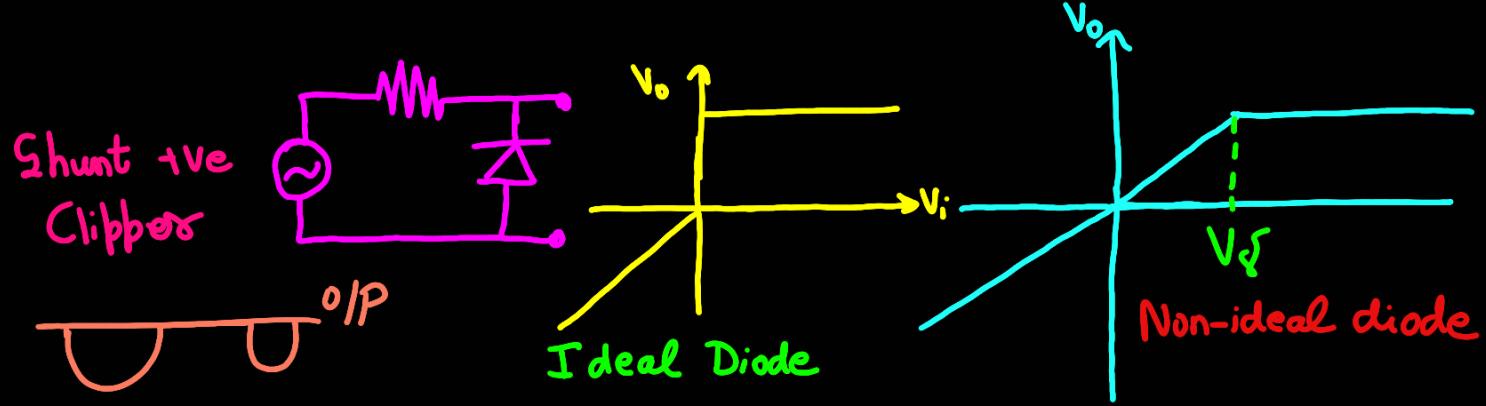


Biased Clipper:-


→ Applying DC voltage to a clipper

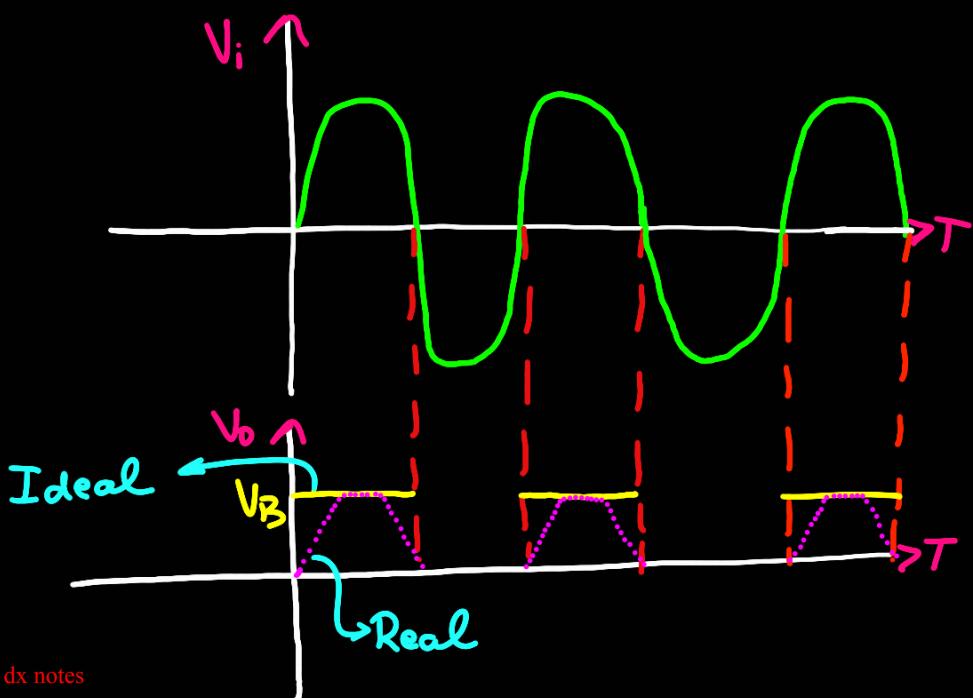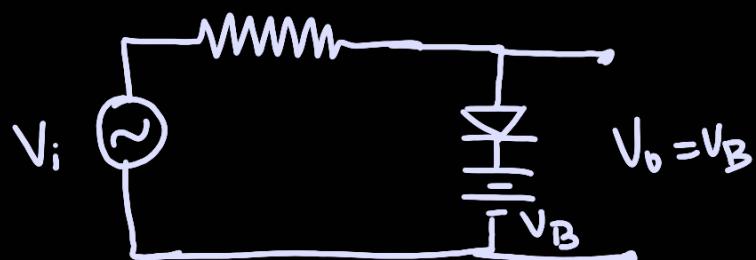

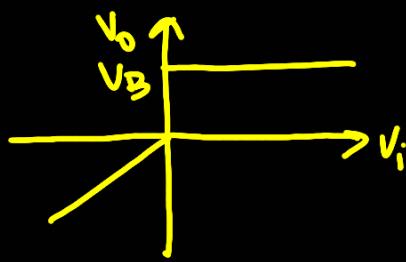Transfer characteristics of biased clipper:-





Ideal diode

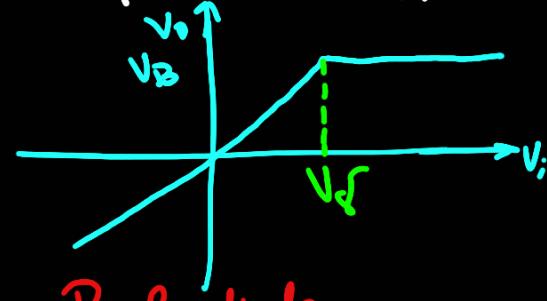

Real diode

Double ended biased clipper:-

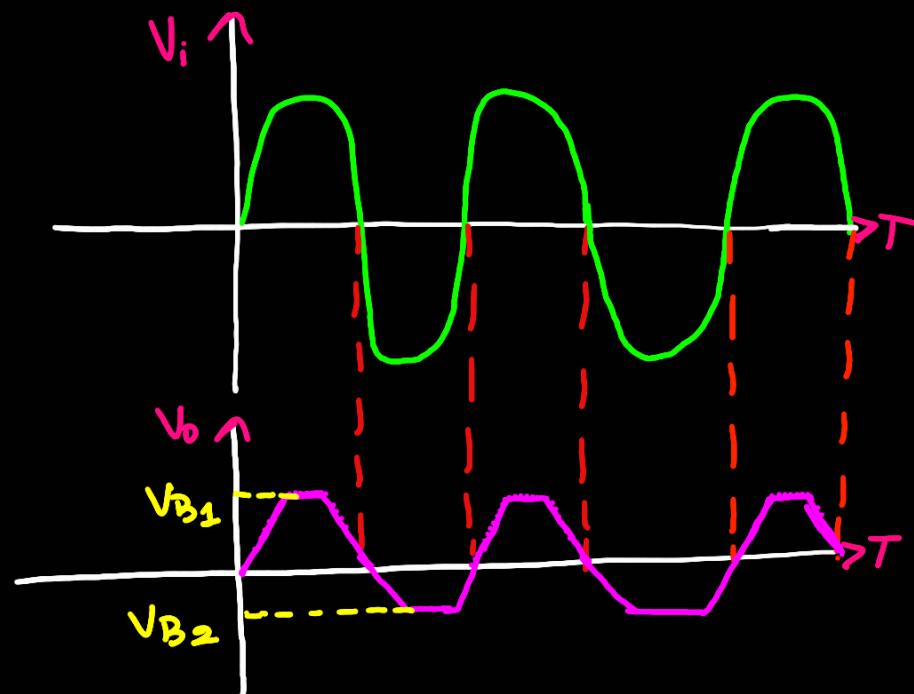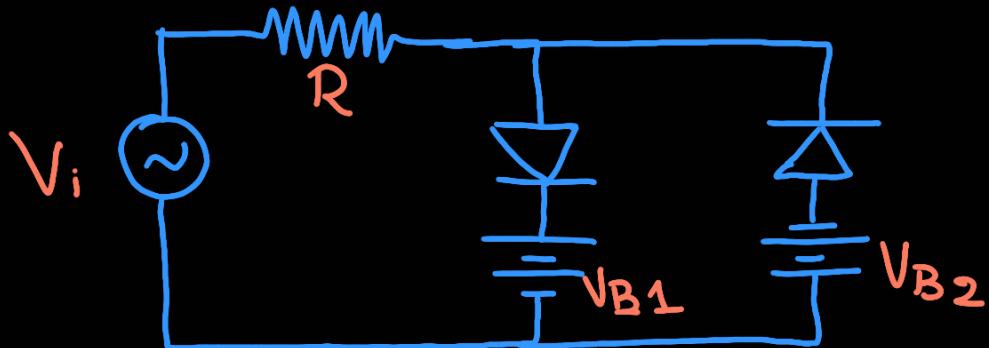

Clamper:-

Accumulation ↑


Capacitor

→ Clamper ckt add / insert / shift the voltage


→ A.K.A DC restorer circuits

→ Clamper can be +ve or negative

* Positive clamer:-

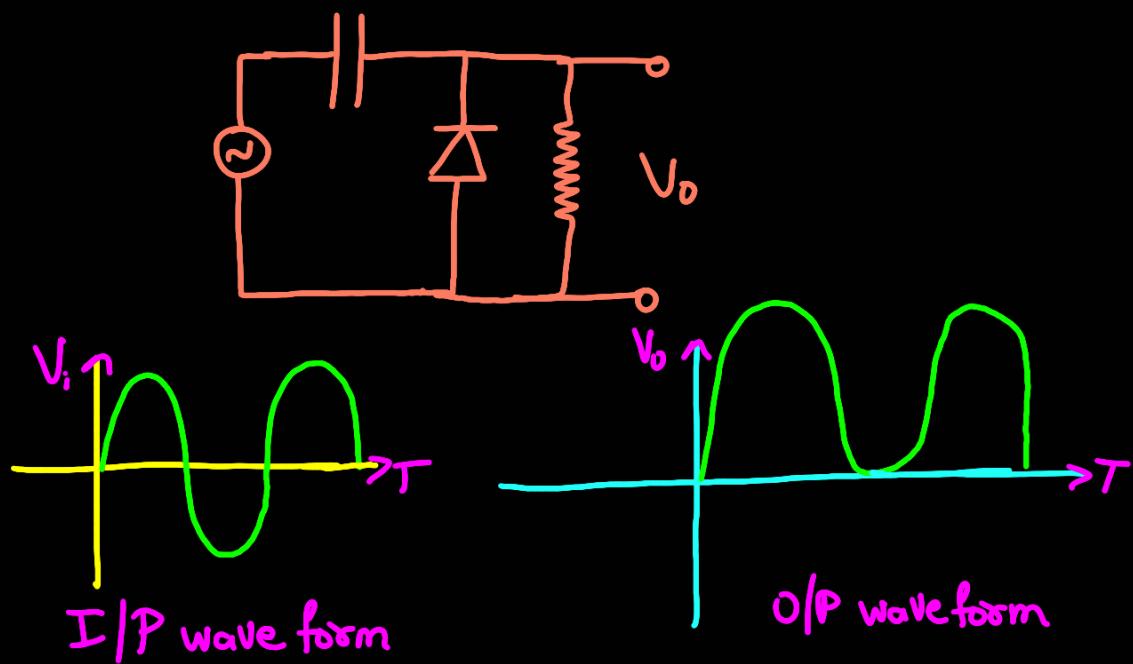

* Negative Clamer:-

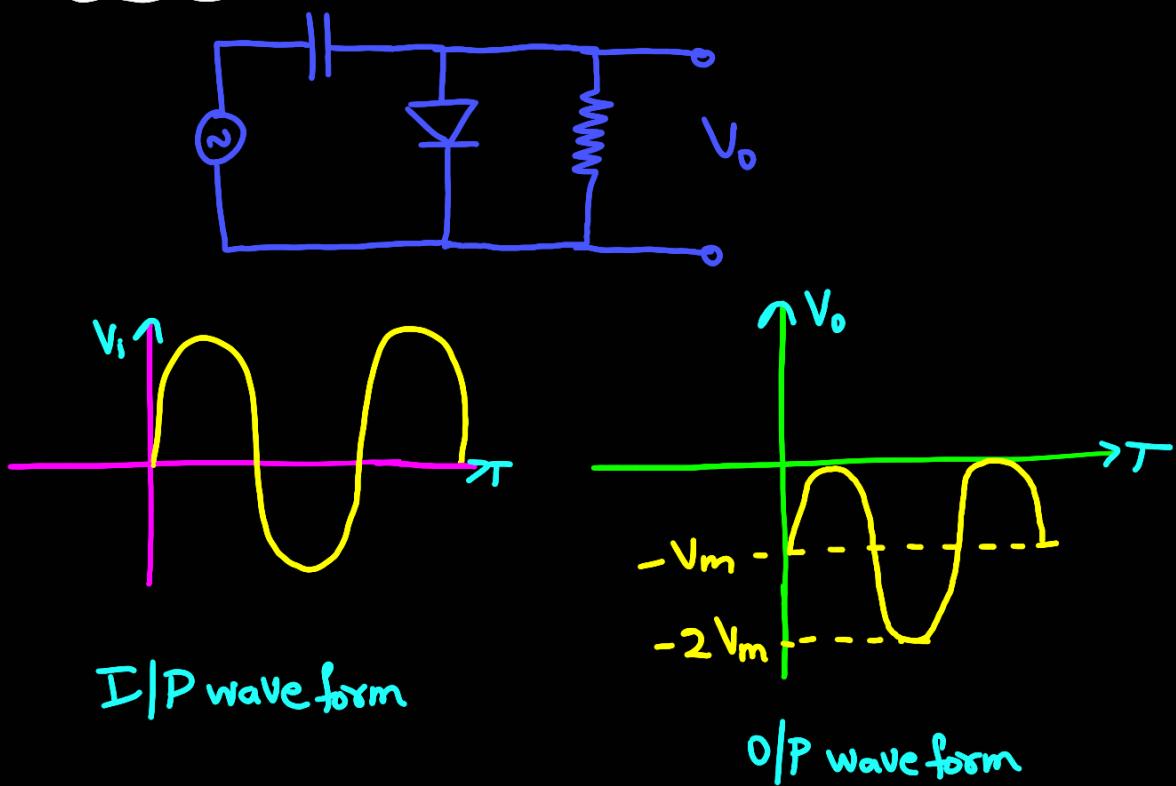

Varactor Diodes:-

P-N j^n diodes

Special diode in which internal capacitance changes with applied reverse bias voltage

AKA:- Varicap diode

Variable Capacitor

Varactor


Variable Reactance

* Ckt Symbol:- 

* Understanding parallel plate capacitor

$$\text{Capacitance} \rightarrow C = \frac{\epsilon A}{d} \rightarrow \text{Permittivity Area}$$

Distance b/w plates

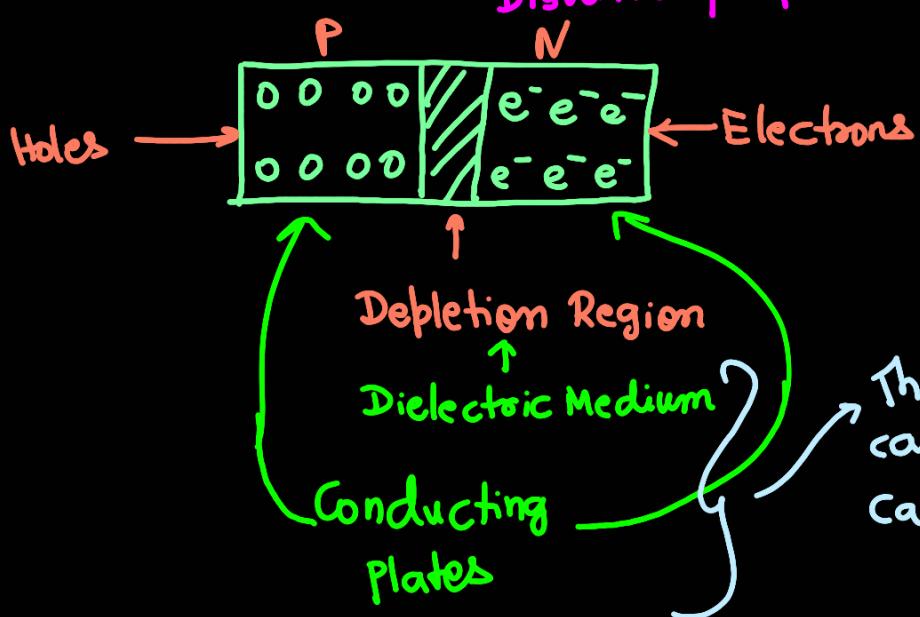

Thus, this P-N j^n can behave as a capacitor

$$C \propto \frac{1}{d}$$

\uparrow in Reverse bias Voltage $\Rightarrow \uparrow$ the width of the depletion layer


n depends
on doping
profile

$$C = \frac{C_0}{\left[1 + \sqrt{\frac{V}{V_f}}\right]^n}$$


$V \rightarrow$ Applied R.B
 $V_f \rightarrow$ F.B voltage of diode
 $C_0 \rightarrow$ Capacitance of diode when unbiased

Based on doping profile there are types of varactor diodes

Abrupt Varactor diode $n=1/2$

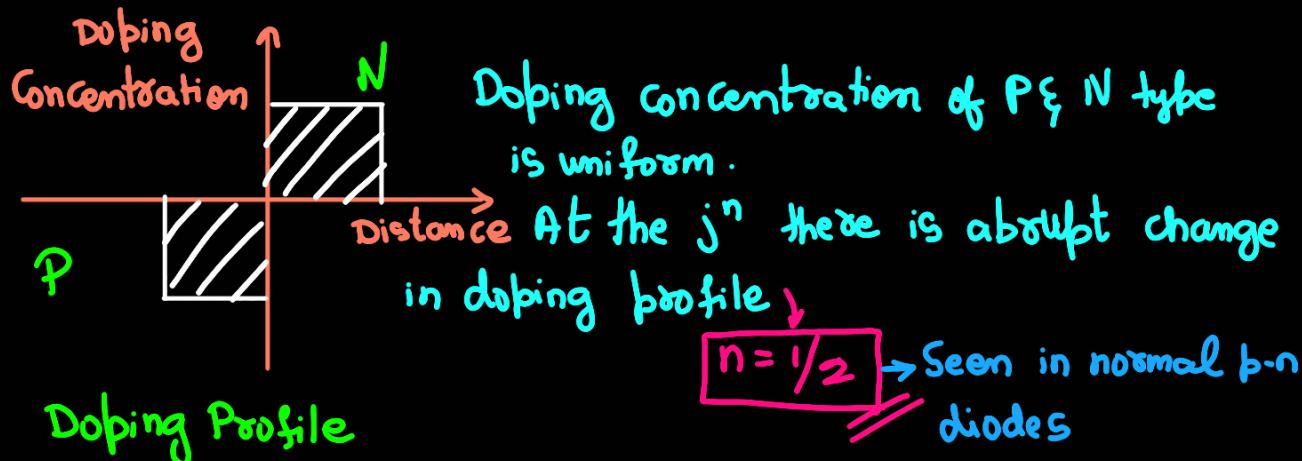

Hyper Abrupt Varactor diode :- $n=2$

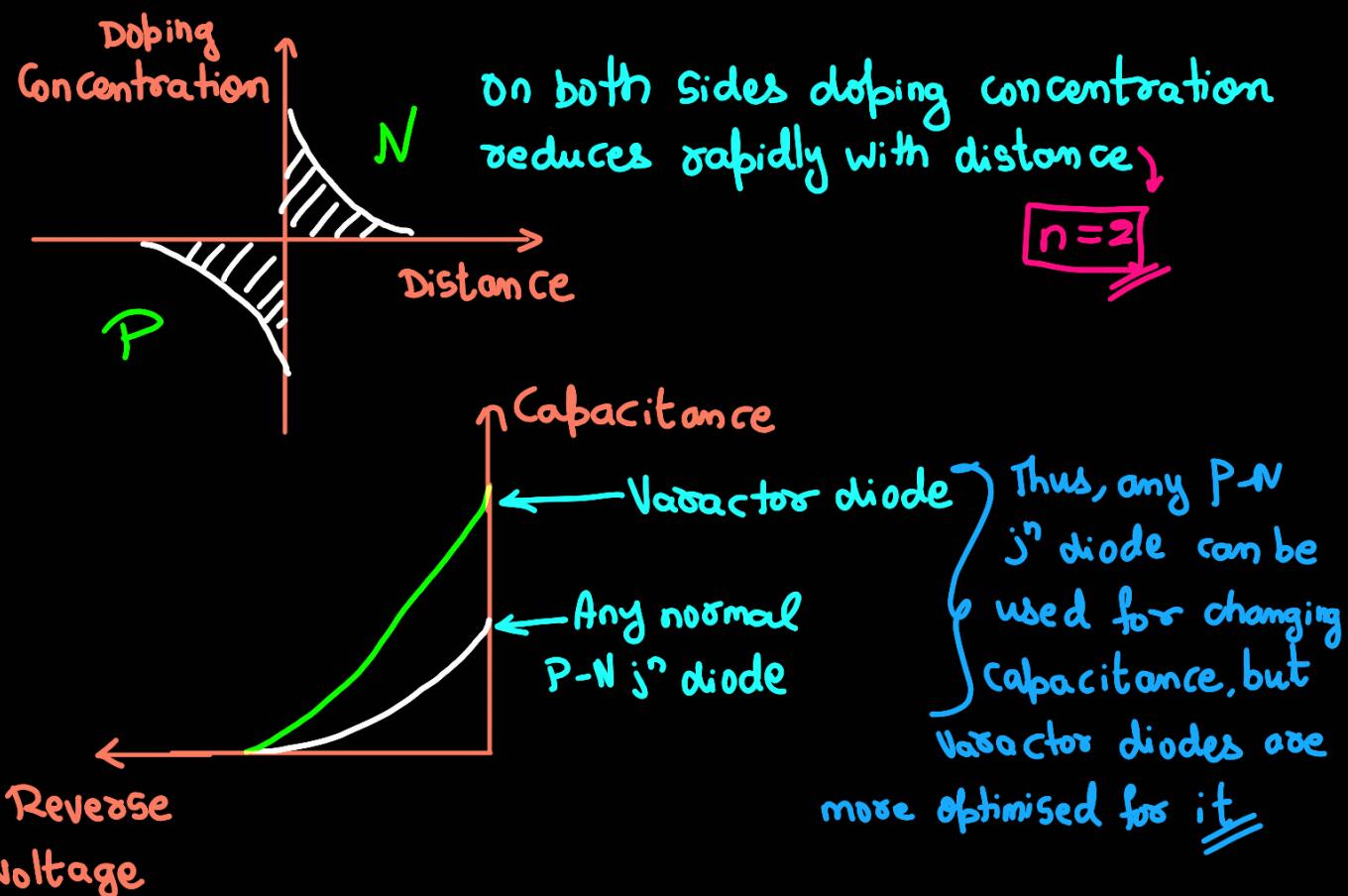

Equivalent Ckt:-

At low freq


At high freq

Reverse Resistance ^{in M-S2 → High to avoid leakage current}

* Low freq:-



\Rightarrow

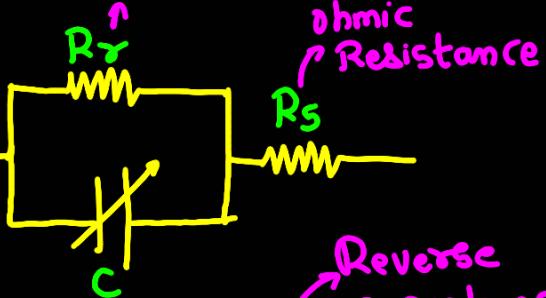


* High freq:-



\Rightarrow L_p

Parasitic Inductance

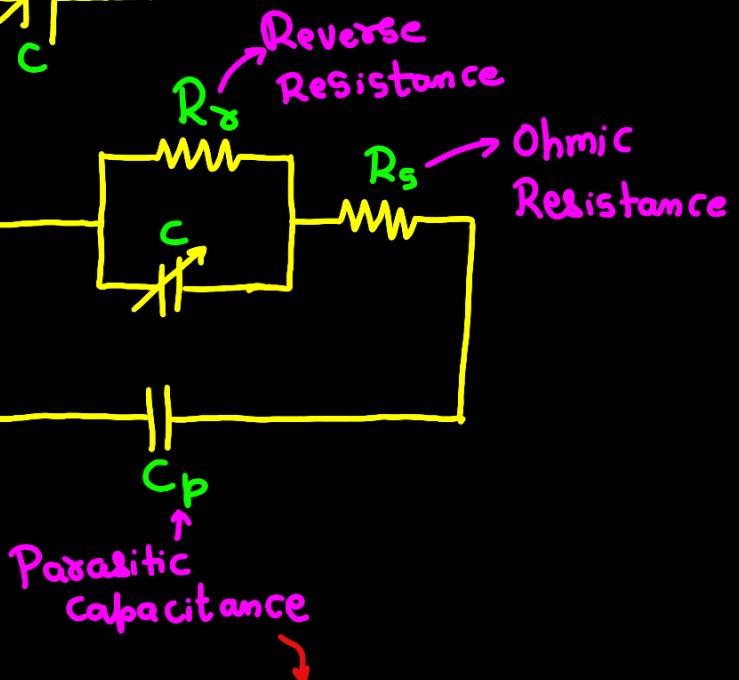Unwanted Inductance
that arises from the
leads and internal
connections of varactor diode



Unwanted capacitance that
exists b/w terminals of
varactor diode

Applications:- Used in tuning ckt

In RF Filters

In Frequency & Phase modulators

OR

Refer below notes for Varactor
Diode

Varicap Diode




- A special diode that uses transition capacitance property i.e. voltage variable capacitance.
- It works under Reverse-Bias conditions
- Under R.B., holes of p-region are attracted to -ve terminal & electrons of n-region are attracted to +ve terminal creating a region devoid of charge carriers. This region behaves as the dielectric of the capacitor
- The Junction capacitance of the diode is inversely proportional to width of depletion layer

$$C_j = \frac{C_{j0}}{(V_b - V)^m}$$

- $g \rightarrow$ diode capacitance
- $c \rightarrow$ unbiased diode capacitance
- $V \rightarrow$ voltage applied
- $V_b \rightarrow$ barrier potential
- $m \rightarrow$ constant depending upon material
- $K \rightarrow$ constant = 1

Voltage - Capacitance Curve

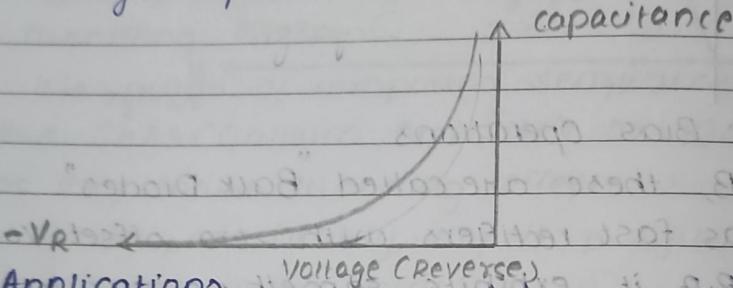


Applications

- Tuned circuits
- FM modulators
- Automated freq. control device
- Adjustable bandpass filters
- parametric amplifiers
- Television receivers

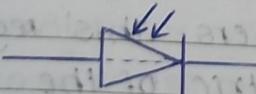d. Briefly Explain LED, OLED & photo diode

→ Photo Diode


It's a p-n junction device whose region of operation is limited to reverse bias region.



"Principle of Operation"


- Photo diode is a type of a photo detector capable of converting light into either current or voltage.

- Photodiode is designed to operate in RB where the depletion region is large.
- When light is incident through glass window on the pn junction diode, photons in the light bombard the p-n junction and some energy is imparted to the valence e⁻'s.
- These valence e⁻s break covalent bonds & become free. Thus more e⁻-hole pair is generated. Thus with increase in minority charge carriers, RB current increases.

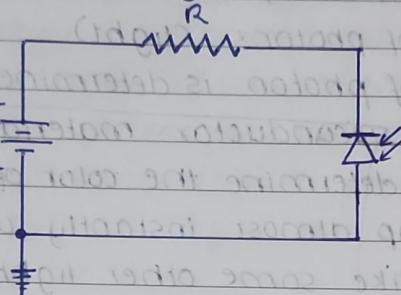

characteristics of photo diode

On

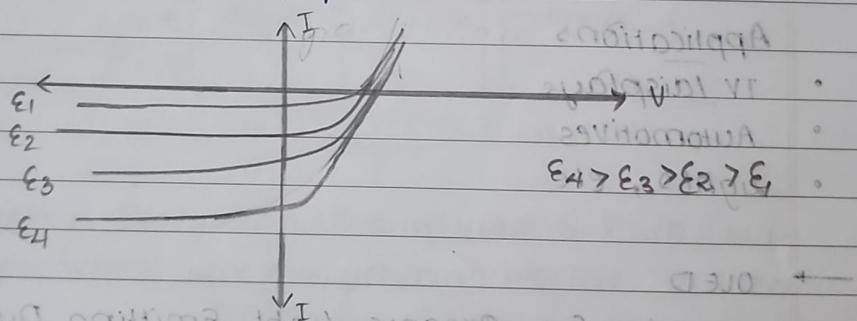

→ LED (Light Emitting Diode)

It's a special heavily doped pn junction diode that emits spontaneous radiation when forward biased.



- When a forward bias is applied across LED, electrons in the valence band gain enough energy to move to the conduction band. This process is known as electron injection.
- Simultaneously holes are created in the valence band.
- The injected electrons in conduction band recombine with the holes in valence band. When they recombine, electrons release energy in the form of photons (light).
- The energy of photon is determined by the bandgap of semiconductor materials and doping levels determine the color of the light.
- LEDs light up almost instantly when a voltage is applied, unlike some other lighting technologies that may have warm-up time.

Applications

- TV Displays
- Automotives
- Lights, etc.

→ OLED

- Stands for Organic Light Emitting Diode
- OLED is an advanced display technology made from thin films of light-emitting organic materials.
- Unparalleled image quality
- Flexible displays / transparent displays

Working

- * OLEDs are made by placing a series of organic films b/w two conductors. When electric current is applied, a bright light is emitted.
- * A simple OLED is made up of six layers. On top and bottom there's the glass/ plastic substrate. In b/w them, there's a cathode (-ve term) & Anode (+ve term). In b/w Cathode & Anode are two layers made from organic molecules called the emissive layer (where light is produced and is next to cathode), usually made of poly fluorine & conductive layer (next to anode) made of poly aniline.
- * holes in conduction layer recombine with e^- in emissive layer and light is produced in emissive layer.

