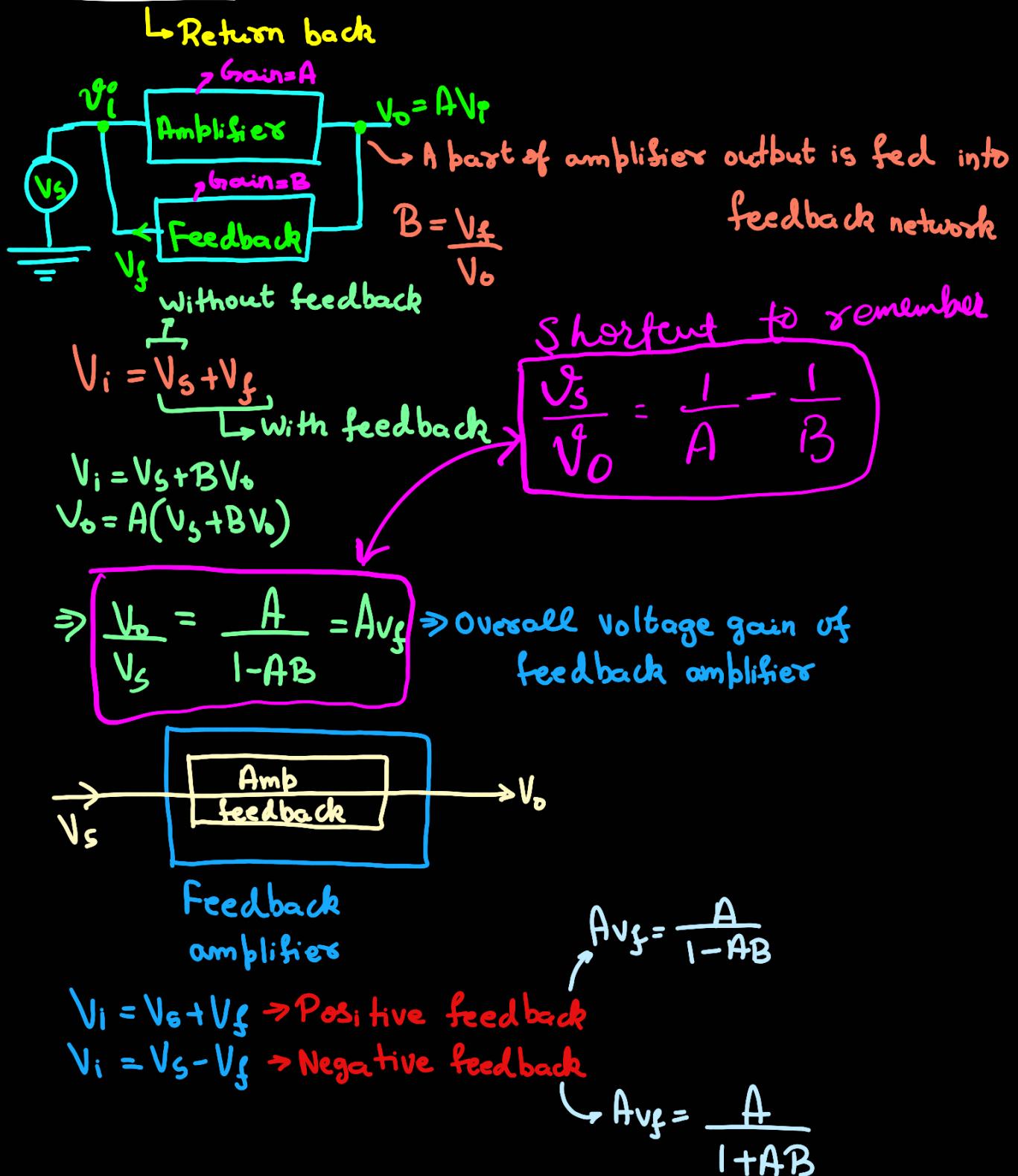


Feedback :-





Types of feedback:-

- ① Negative feedback → Feed a -ve voltage } without coupling
- ② Positive feedback → Feed a +ve Voltage } capacitors in RC coupled amp.

Negative feedback:-


- Feedback in which -ve voltage is fed
- Amplifier gain reduces
- Noise reduces due to reduction in amplifier gain
- Improves the bandwidth
- Amplifiers performance improves due to higher stability

Positive feedback:-

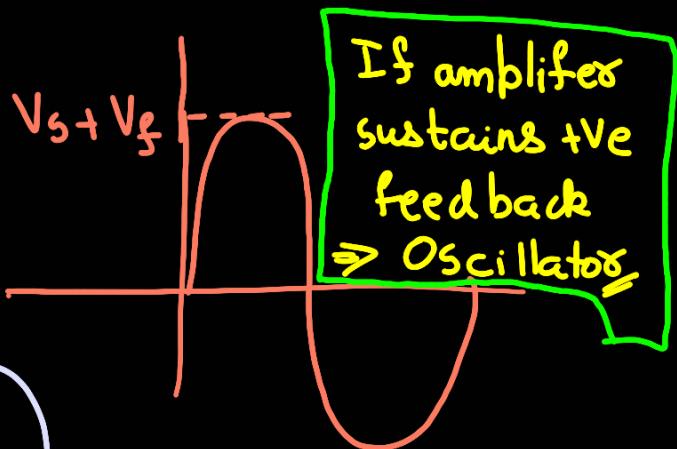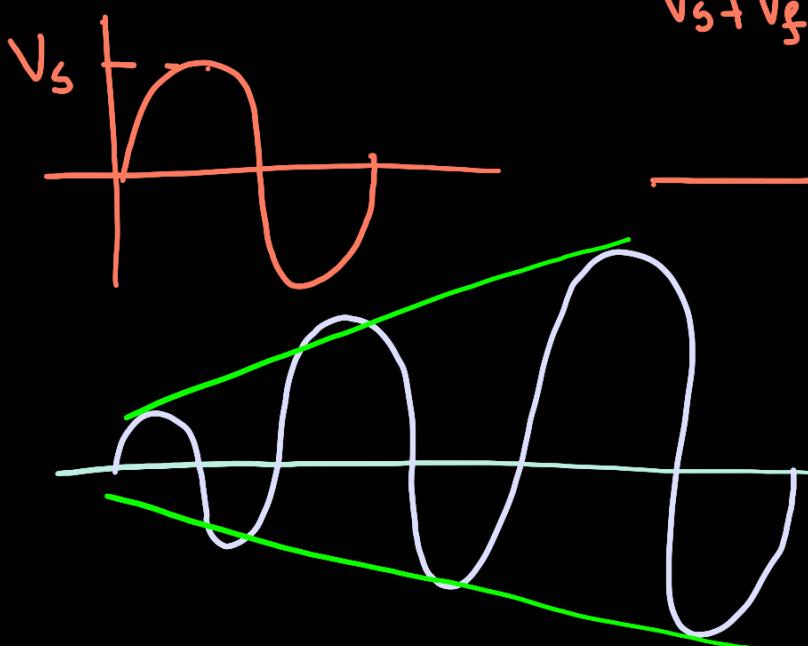

Positive Feedback diverges & O/P becomes unstable

Principles of oscillator:-

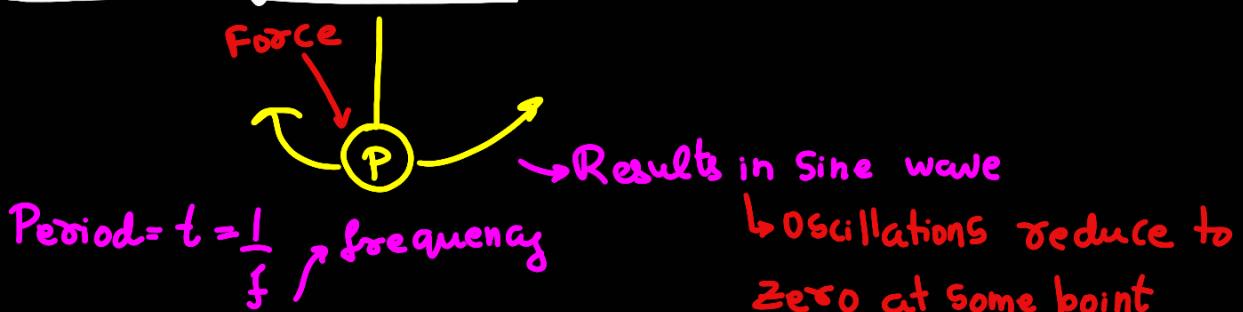


$$\text{Period} = t = \frac{1}{f} \rightarrow \text{frequency}$$

As long as we supply energy regularly to the pendulum, the oscillations will fully continue till the energy supply lasts

This can be achieved in Electronics with the help of a Tank circuit


Tank Circuit:

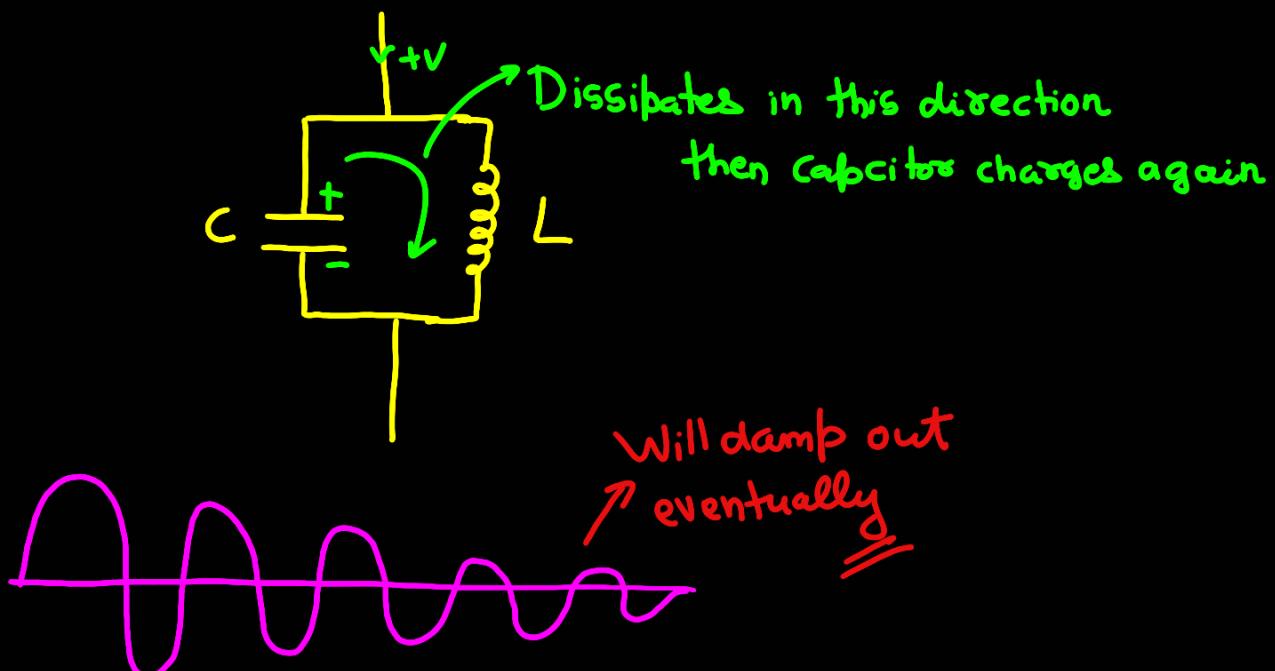An LC parallel ckt is called Tank circuit



$$f = \frac{1}{2\pi\sqrt{LC}}$$

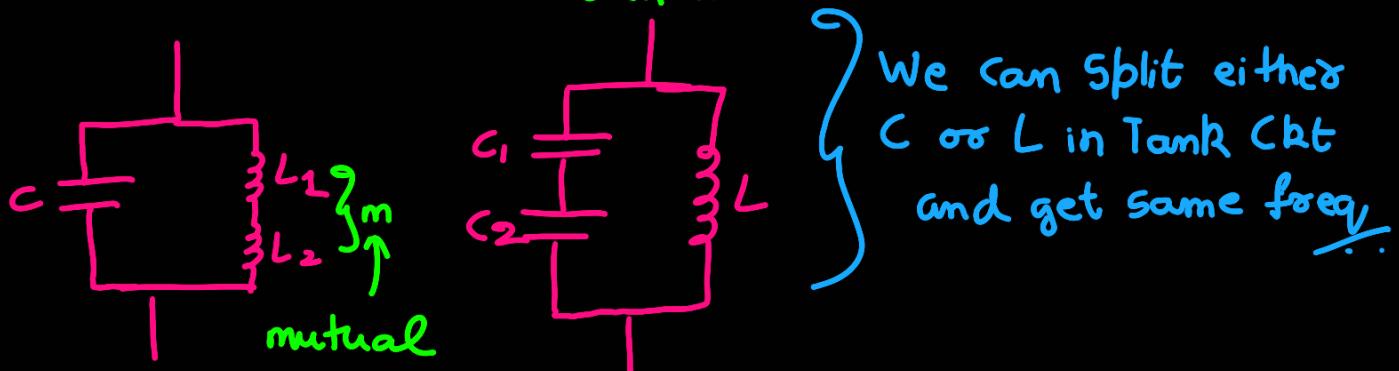
This much voltage must be regularly supplied to sustain output.



$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$L = L_1 + L_2 + 2M$$

Grain = A

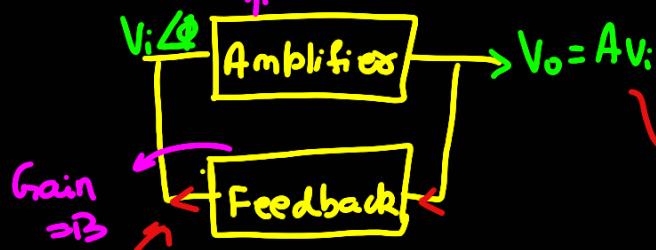

Overall Gain
 $= LoopGain = \alpha \times \beta = 1$

Grain $\leftarrow I$

Always 1

Output out of phase by 180°

Phase Shift of additional $180^\circ \Rightarrow \text{Total } \Delta\phi = 360^\circ$

Conditions for sustained oscillations:-

These conditions are called Barkhausen's criteria

- Loop Gain = 1
- Overall phase shift in the loop must be $0^\circ/360^\circ$

Oscillators:-

An amplifier with +ve feedback network & that can sustain O/P based on Barkhausen's Criteria is called oscillator




Types of oscillators:-

- Hartley oscillator
- Colpitts oscillator
- RC phase shift oscillator
- Crystal oscillator

→ These are Radio freq.
or high freq. oscillators

→ Audio freq. or low freq. oscillators

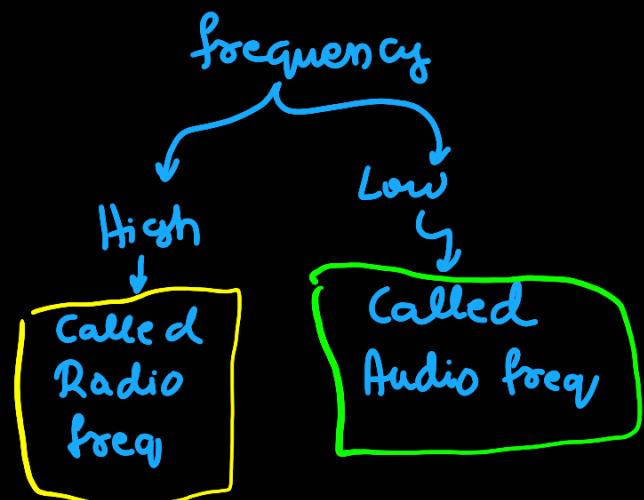


$L \& C$ is not used for low frequency oscillations as the circuit will become lengthy.

Thus only $R \& C$ are used for AF

Hartley oscillator :-

↳ H → Inductance

↳ Split the inductors

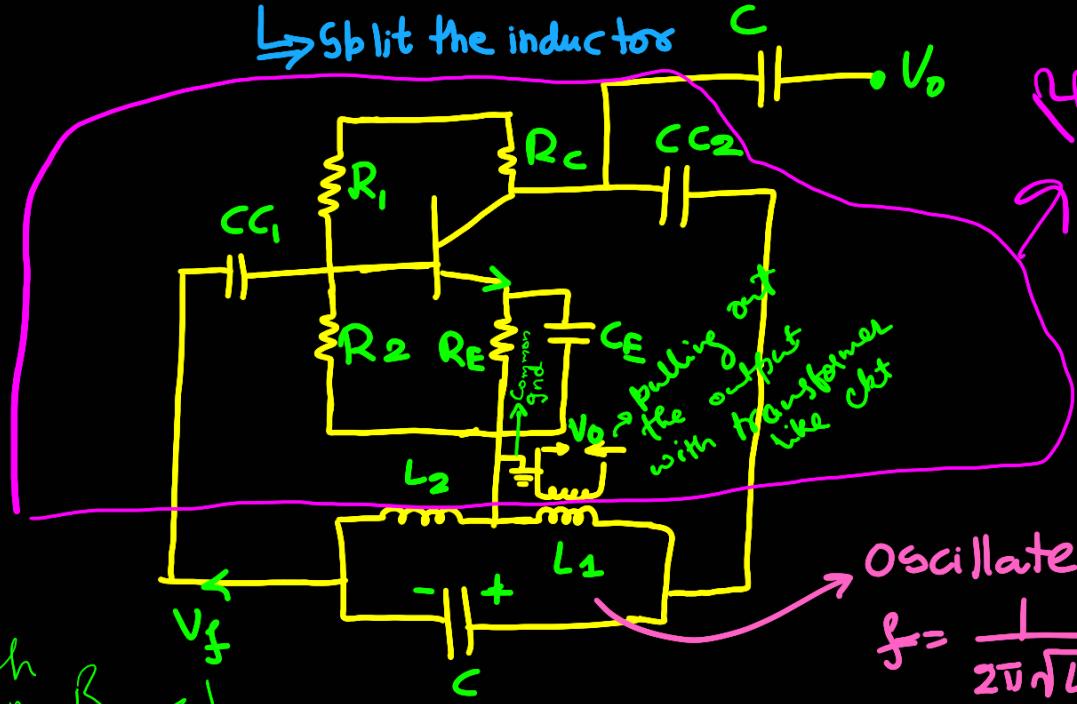

with
gain β

Explain the det → Amp, Tank det, then
output can be taken
before CC_2 or across L_1

To prove Barkhausen Criteria:-

$$1) AB = 1$$

$$2) \text{overall phase shift} = 0^\circ / 360^\circ$$

$$V_o = V_i \underline{180^\circ} (A = 1)$$

$$V_f = V_o \underline{180^\circ} (\beta = 1)$$

$$\text{Wkt, } V_i = V_f \underline{\phi} = V_o \underline{180^\circ}$$

$$\text{but } V_o = V_i \underline{180^\circ}$$

$$\therefore V_i = V_f \underline{180^\circ} \underline{180^\circ} \Rightarrow V_i = V_f \underline{360^\circ} \rightarrow \text{Criteria ①}$$

$$B = \frac{\text{Op voltage}}{\text{IP voltage}} = \frac{V_f}{V_o} = \frac{X_{L_1}}{X_{L_2}} = \frac{\omega L_1}{\omega L_2} \hookrightarrow$$

$$A = \frac{L_2}{L_1} \Rightarrow A = \frac{1}{B} \Rightarrow AB = 1$$


2nd Criteria

Colpitts oscillator:-

↳ C → capacitance

↳ Split capacitor

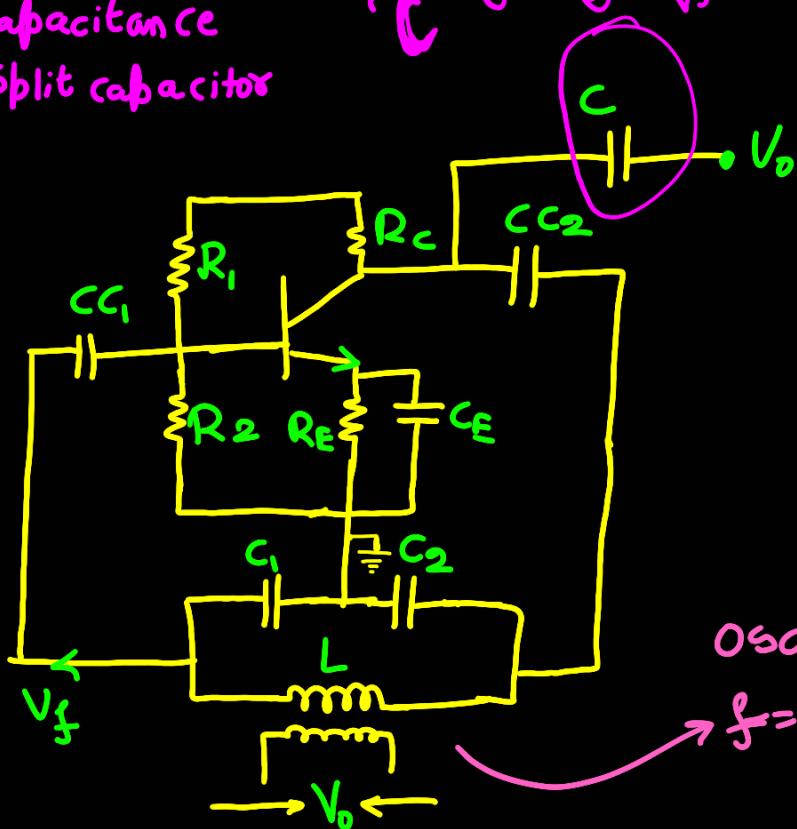This 'C' for ↓ i.e. reducing noise
Netter output



Oscillate at freq,
 $f = \frac{1}{2\pi\sqrt{LC}}$
 where $C = \frac{C_1 C_2}{C_1 + C_2}$

Explain the dat → Amp, Tank dat, then
 output can be taken
 before CC2 or across L

To prove Barkhausen Criteria:-

$$1) AB = 1$$

$$2) \text{overall phase shift} = 0^\circ / 360^\circ$$

$$\left. \begin{array}{l} V_f = i X_{C_1} = \frac{i}{\omega C_1} \\ V_0 = i X_{C_2} = \frac{i}{\omega C_2} \end{array} \right| \quad B = \frac{V_0}{V_f} = \frac{\frac{i}{\omega C_2}}{\frac{i}{\omega C_1}} = \frac{C_1}{C_2}$$


If $A = \frac{C_2}{C_1}$ then oscillations will be sustained

Phase diff expl^n same \Rightarrow Prove Barkhausen Criteria

#RC phase shift oscillator:-

360° overall shift

Feedback network

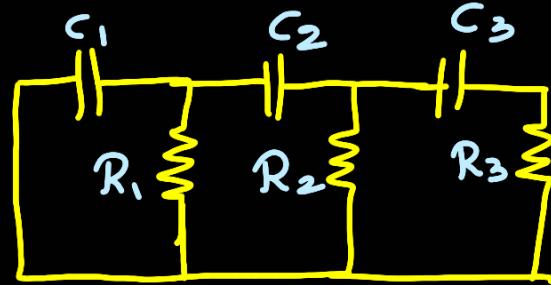

At eq^m frequency,
phase shift is 60° in
each loop.

\Rightarrow Max phase shift = 180°


$$\text{Eq}^m \text{ frequency } f = \frac{1}{2\pi RC\sqrt{6}}$$

$$R_1 = R_2 = R_3 = R$$

$$C_1 = C_2 = C_3 = C$$

for other freq., the phase shift in each loop goes to 90°, So $90 \times 3 = 270$

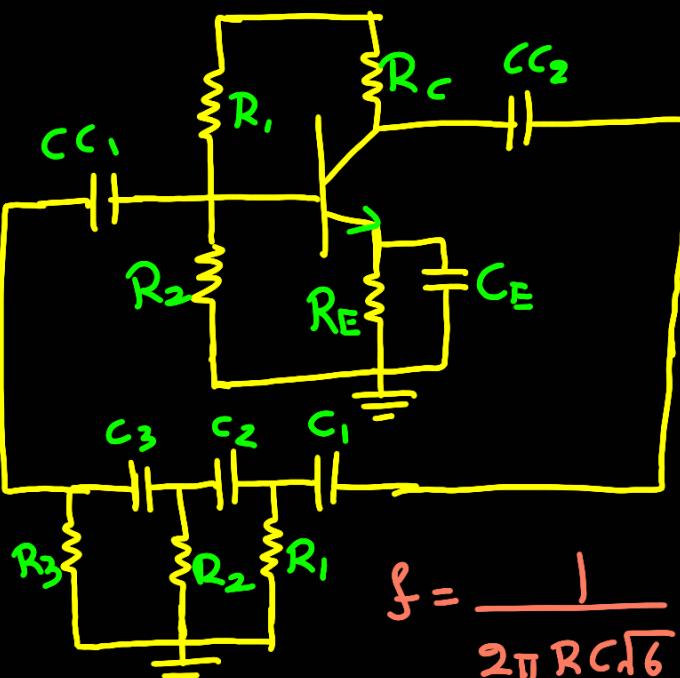\therefore freq. is maintained @ Equilibrium freq



$$f = \frac{1}{2\pi RC\sqrt{6}}$$

At $f \Rightarrow$ phase shift in each RC network is 60°. \therefore Total feed back network phase shift is 180°

Amplifier $\beta S = 180^\circ \Rightarrow$ Total = 360° \rightarrow Barkhausen Criteria 1 satisfied

Barkhausen

Criteria 1 satisfied

The gain of the 3 RC network is $\perp \Rightarrow B = \frac{1}{29}$

\therefore If $A = 29$, then $AB = 1 \Rightarrow$ B.C 2

Satisfied

Crystal oscillator:-

Made of quartz \rightarrow Property \rightarrow Piezo electric property

Application of pressure creates electrical energy


Application of pressure creates electrical energy


Mechanical energy is converted to electrical energy and vice-versa

We need the crystal to vibrate in order to generate oscillations.


We now apply variable voltage to the crystal to produce vibrations, these vibrations then create oscillatory current!

Electrical Equivalent ckt of crystal :-

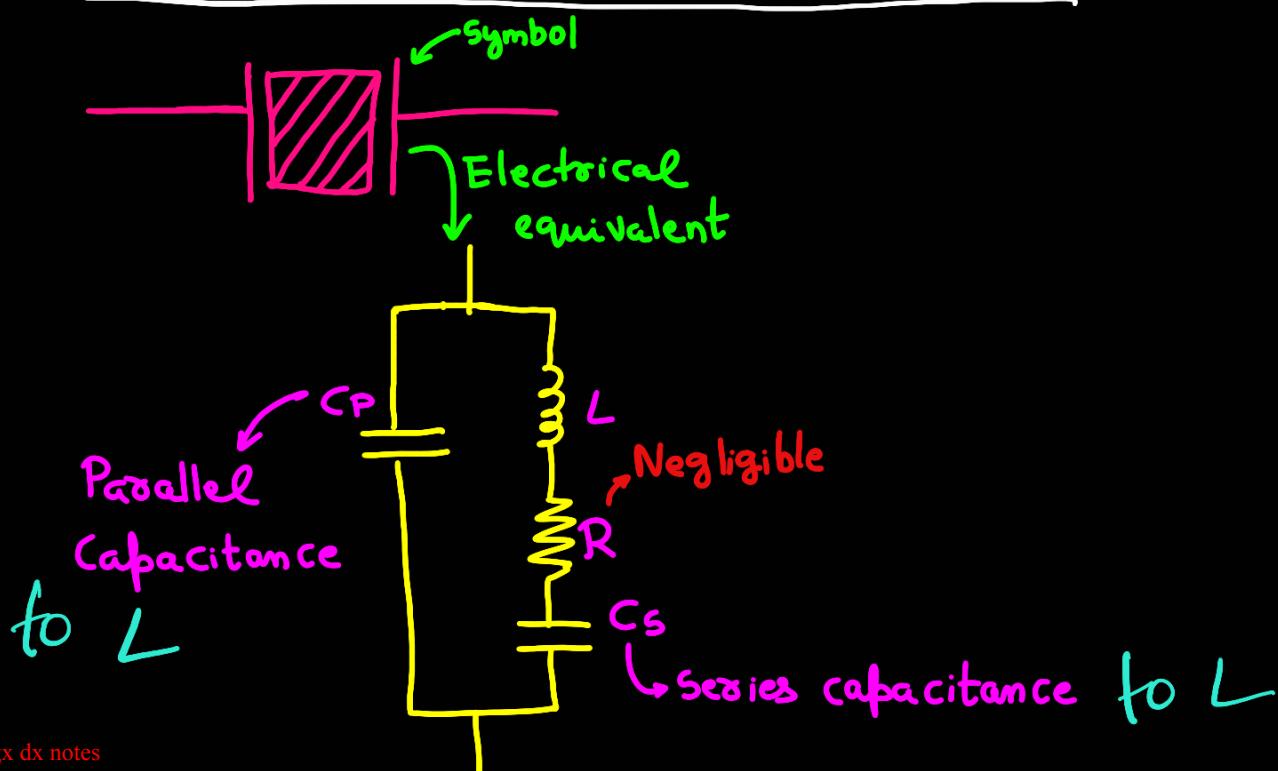

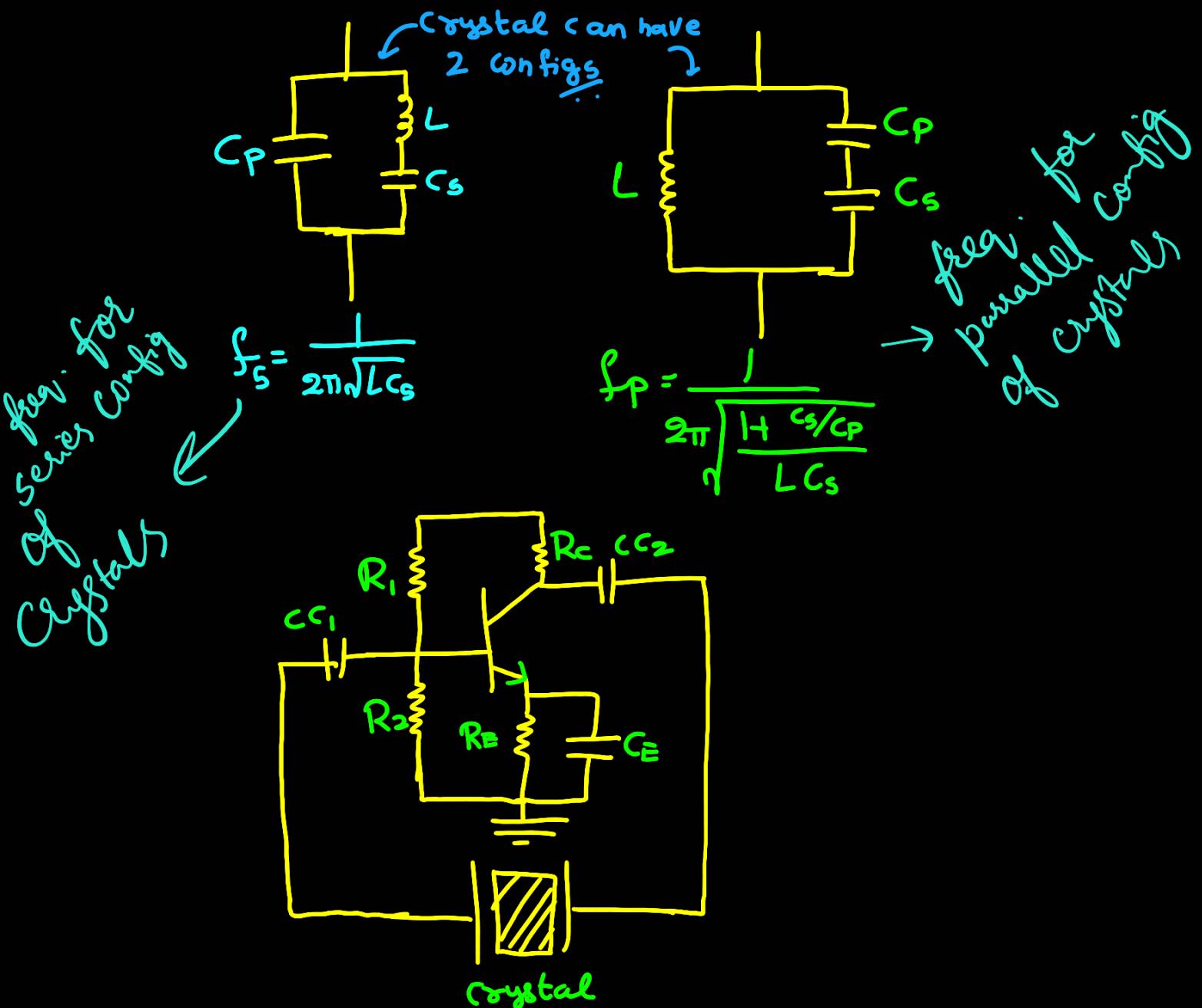

Impedance characteristics of crystals:-

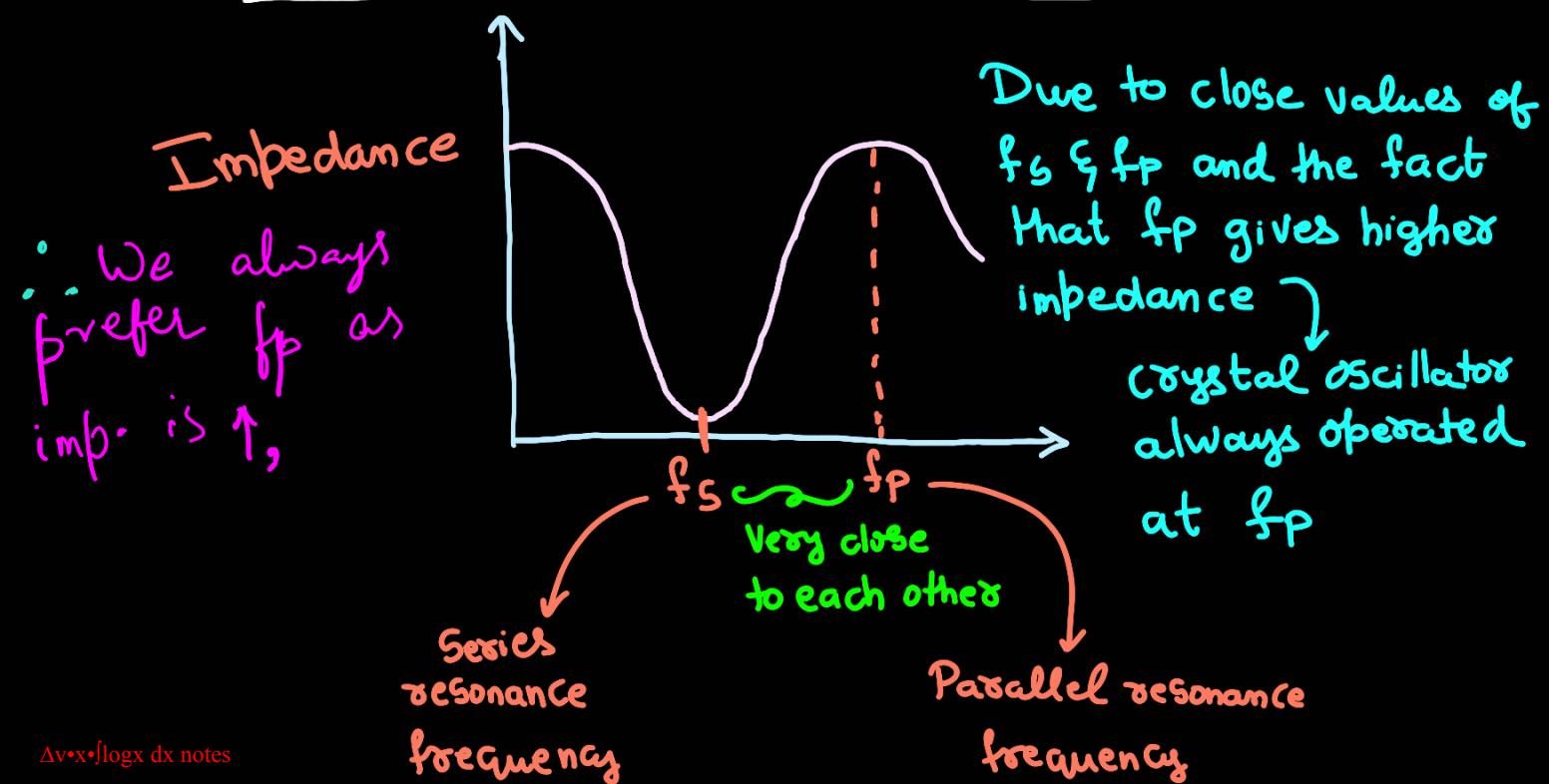

* The material size is almost constant for variable appⁿ of temp, thus f is stable

Unlike in LC, in which L & C are likely to change, thus freq, may be unstable & need more economy to stabilise


∴ Crystal oscillator is more stable

Additional points:-

* RC not preferred for high freq oscillators as RC becomes too low.

* To avoid power dissipation we replace R_c in amplifier with an inductor called Radio Frequency coil (RFC)

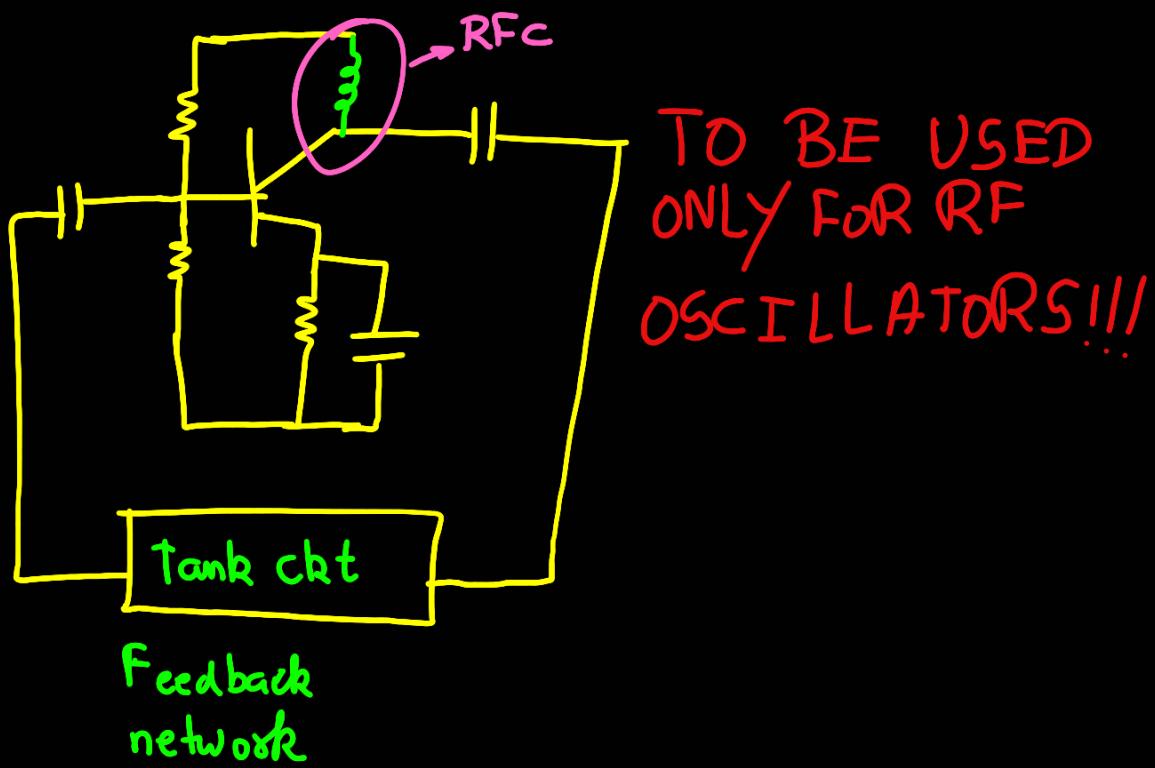Advantage:- DC power in the collector resistor reduces, thus not draining input very quickly.




Operational Amplifiers:-

Gives large output



May not be enough

∴ Cascade multiple amplifiers together

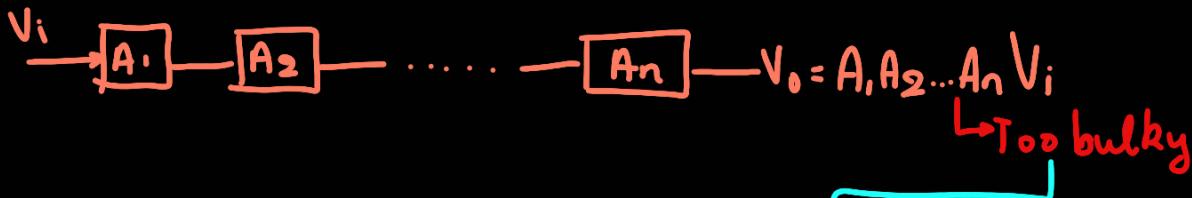

We need something just like this
but a Single integrated circuit

Op-Amp :-

↳ Has a very high gain integrated into a single circuit

Operations:-

Mathematical (Arithmetic)

Logical

Relational

coz its continuous

↳ Analog


Circuit

↳ Op-Amp is

a linear circuit


Cancels
the Common
DC voltage

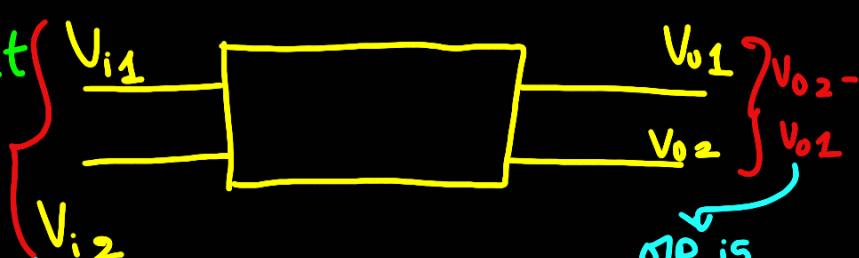Has a very high gain &
capable of performing certain
operations like mathematical, logical
& relational.



∴ Differential I/P & Differential O/P

Different amplifiers :-

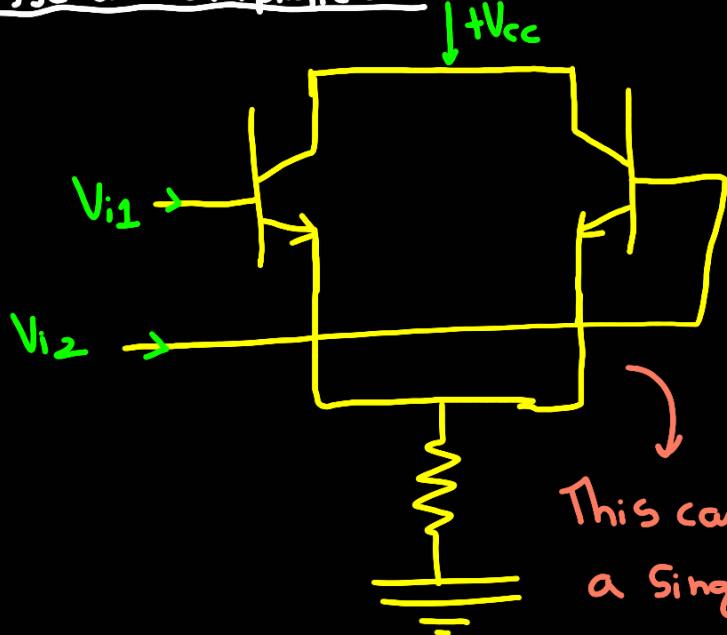


Capacitors &
Biasing resistors
eliminated

This can be integrated into
a Single chip.

Cascading

Symbol:-

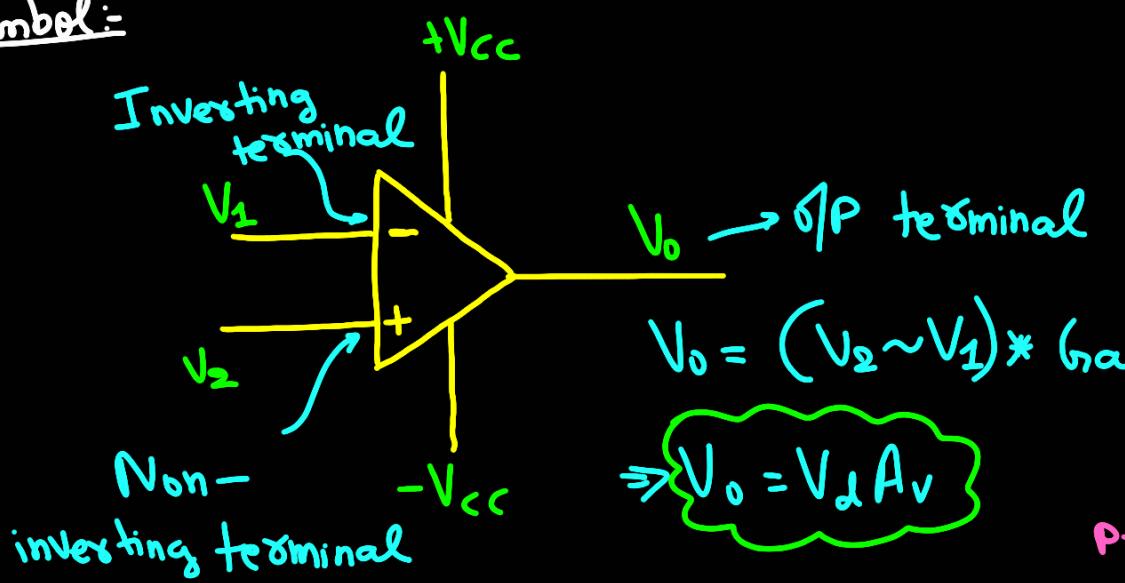


$$V_o = (V_2 - V_1) * \text{gain}$$

$$\Rightarrow V_o = V_d A_v$$

Provides
current &
Voltage swing
by the load

Block diagram of op-Amp:-

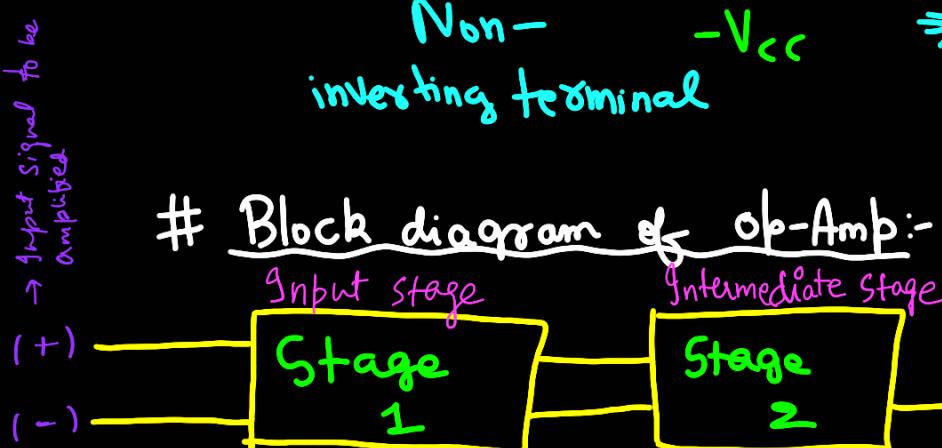

Level
Shifters

Power
amplifiers

1. It's a differential amplifier
2. It's a dual input, balanced output Diff. Amp. (*DUAL O/P*)
3. Rejects noise
4. This stage also provides high I/P impedance
5. Provides high voltage gain

1. Dual I/P (balanced) and unbalanced O/P amplifier.
2. Provides very high voltage gain

1. The O/P of stage 2. i.e I/P of stage 3 is above GND as direct coupling is used.
2. Level 3 (level shifter) is used to sift the O/P of level 2 downwards (wrt GND)

1. Also called as push pull amplifier
2. Increase the O/P voltage swing
3. Improves current supplying capabilities
4. Provides Min. O/P impedance

Voltage Transfer characteristics

Ideal Op-Amp VTC & its characteristics:-

★ ∞ i/p impedance \downarrow
Ideally no loading needed

★ Zero o/p impedance \downarrow
O/P can drive ∞ no. of other devices

★ ∞ Bandwidth \downarrow
So, that any freq. can be accepted by the ideal op-amp

★ ∞ Voltage gain

★ Perfect Balance, i.e. input offset voltage = 0
(If no i/p no o/p at all IDEALLY)

★ ∞ CMRR (Common Mode Rejection Ratio)

Normal difference \rightarrow When there is a
voltage \downarrow $\frac{V_o}{R_f + R_s} \approx \frac{V_o}{R_s}$

Differential Gain

Common Mode Gain

If both the input signals are same or grounded, then diff. i/p is 0, \therefore the output is also 0 ideally, but $\neq 0$, practically

★ ∞ Slew rate \rightarrow Rate of change of o/p voltage w.r.t time $= \frac{dV_o}{dt}$

(Tells us how fast the amplification process takes place)

+ve saturation voltage ($+V_{sat}$)
and it's less than or equal to $+V_{cc}$
*NOTE: Similarly for $-V_{sat}$ & $-V_{cc}$ *

@ Saturat' region
 \rightarrow It becomes an oscillator (constant gain)

Note: For an amplifier gain must keep on changing

@ Saturat' region
 \rightarrow It becomes an oscillator (constant gain)




Linear region
Gain varies in this region only.
Amplifier works in this region

Neg feedback



$A = \infty$
Disadv: No use

Gain can be

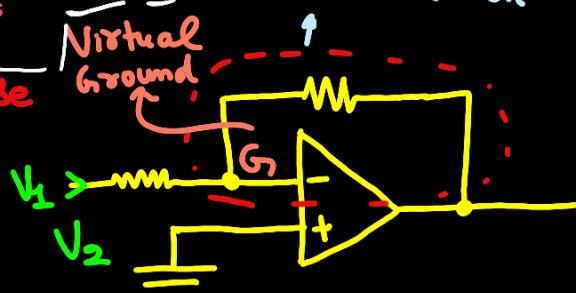

★ Op-Amp is amplifier with -ve feedback

reduced using -ve feedback


$$O/P = -V_o$$

$$I_S = -I_1$$

O/P is always 180° out of phase

Applications of Op-Amp:-

① Inverting Amplifiers:-

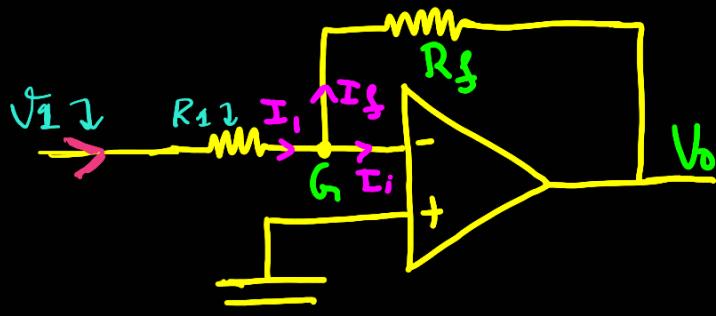

$$V_0 = A_v V_1$$

$$I_1 = \frac{V_1 - V_G}{R_1}$$

$$V_G = 0$$

$$I_1 = \frac{V_1}{R_1}$$

$$I_1 = I_i + I_f \Rightarrow I_1 = I_f$$

$$I_f = \frac{V_G - V_o}{R_f} = -\frac{V_o}{R_f}$$

$$-\frac{V_o}{R_f} = \frac{V_1}{R_1} \Rightarrow V_o = -\frac{R_f}{R_1} V_1 \rightarrow \text{O/P voltage}$$

$A_v = -\frac{R_f}{R_1}$


→ Gain

* R_f : feedback resistance

* I_i : Inverting current

* I_1 : Net current

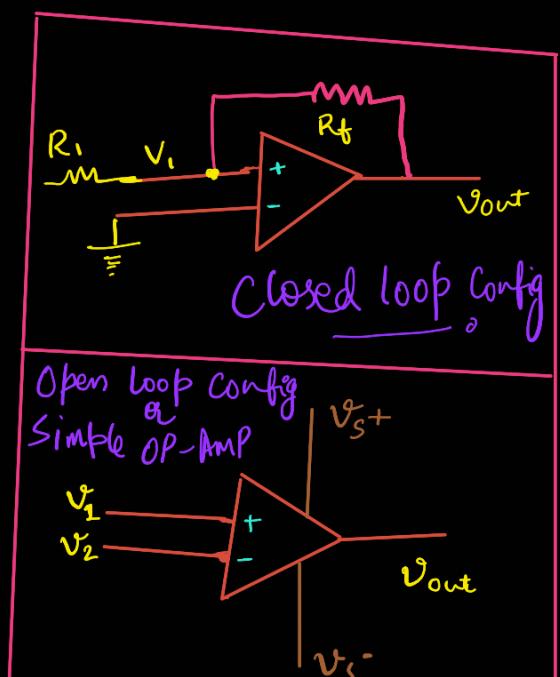- 1. Does not exist in electrical ckt's, it exists only in Electronic ckt's (op-amps)
- 2. Node whose voltage is zero but not connected to GND physically or mechanically.




The open loop gain is extremely high, and because of such high gain the OP AMP becomes unstable, so in order to avoid such conditions we connect a resistor (Rf) from output back to the input (closed loop OP AMP) to lose some gain, this helps us in reducing and controlling the gain. It depends on the value of the resistor (Rf).

Therefore, closed loop OP AMP is more controlled than open loop OP AMP

O/P is inverted by a phase shift of 180°

Non-inverted amplifiers:-

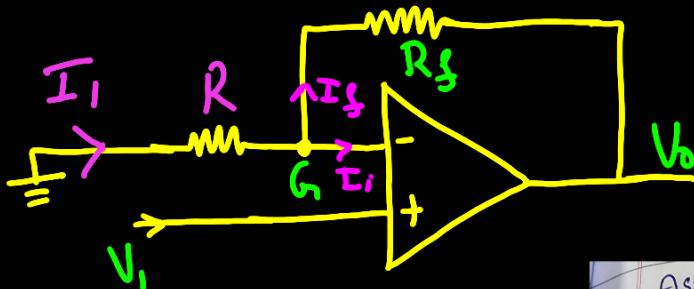

Follow same procedure for $V_o \& A_v$

$$V_o = \left(\frac{R_f}{R_i} + 1 \right) V_i \quad \rightarrow \text{O/P voltage}$$

$$A_v = \frac{R_f}{R_i} + 1 \quad \rightarrow \text{Gain}$$

Assume $V_{C_1} = V_i \rightarrow ①$
Now,
 $I_s = I_i + I_f$
 $I_s = I_f \rightarrow ② \quad (\text{If } = 0, \text{ so T/P Impo} = \infty)$


$$I_f = \frac{V_{C_1} - V_o}{R_f} = \frac{V_i - V_o}{R_f} \rightarrow ③ \quad (\because V_{C_1} = V_i)$$

$$I_s = \frac{0 - V_{C_1}}{R} = -\frac{V_i}{R} \rightarrow ④ \quad (\text{as } V_{C_1} = V_i)$$

from ③, ④ &
 $\frac{V_i - V_o}{R_f} = -\frac{V_i}{R} \Rightarrow -1 + \frac{V_o}{V_i} = \frac{R_f}{R}$
 $\Rightarrow A_v = \frac{R_f}{R} + 1$

**O/P phase shift is $0/360^\circ$

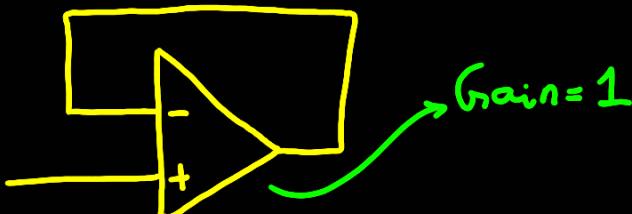Voltage Followers/Unity Gain Amplifiers/Buffer Amplifiers:-



$$\text{Non-inverting amplifier gain} = \frac{R_f}{R_i} + 1$$

$$\text{Eliminating } R_f \Rightarrow A_v = 1$$


$$\therefore V_o = V_i \rightarrow \text{Thus, } V_o \text{ follows } V_i$$

1. In buffer amplifier the O/P voltage follows I/P voltage, i.e. $V_{out} = V_{in}$
2. Loop gain = 1
3. It's a special case of *Non-inverting (+ve)* amplifier so phase of O/P signal is $0/360^\circ$
4. Feedback resistance (R_f) = 0
 $R_1 = \infty$


Application:

1. Adds buffer effect to the ckt
2. Used for impedance matching
3. Acts as an Isolator

Summing Amplifiers :-

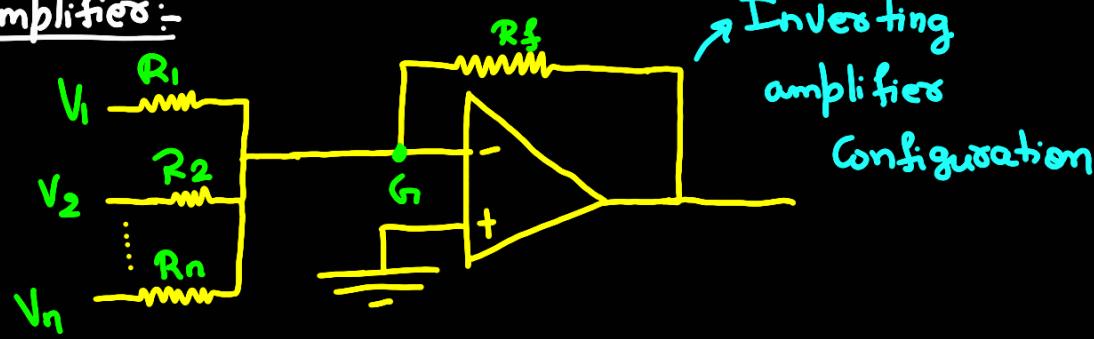

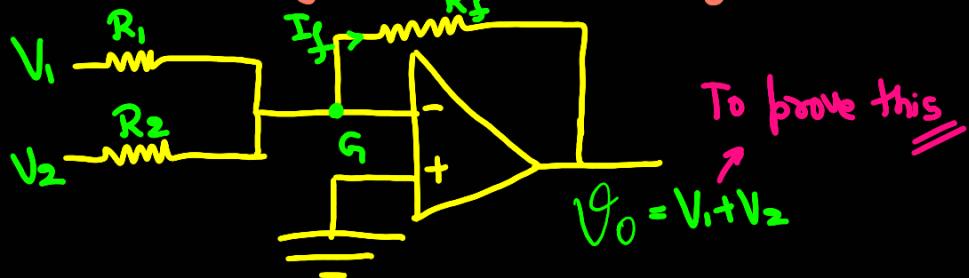For analysis, we consider only $V_1 \& V_2$



$$I_1 = \frac{V_1 - V_G}{R_1} = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2 - V_G}{R_2} = \frac{V_2}{R_2} \quad (V_G = 0)$$

* The sum of currents $I_1 \& I_2$ enters node G

* Since I_i (current into op-amp) is zero $\Rightarrow I_f = I_1 + I_2$


$$I_f = \frac{V_G - V_0}{R_f} = \frac{-V_0}{R_f}$$

$$\frac{-V_0}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$


$$\text{Let } R_f = R_1 = R_2 = R$$

Thus, it can be used as adder circuit

$$\Rightarrow -V_0 = V_1 + V_2 \Rightarrow | -V_0 | = V_1 + V_2$$

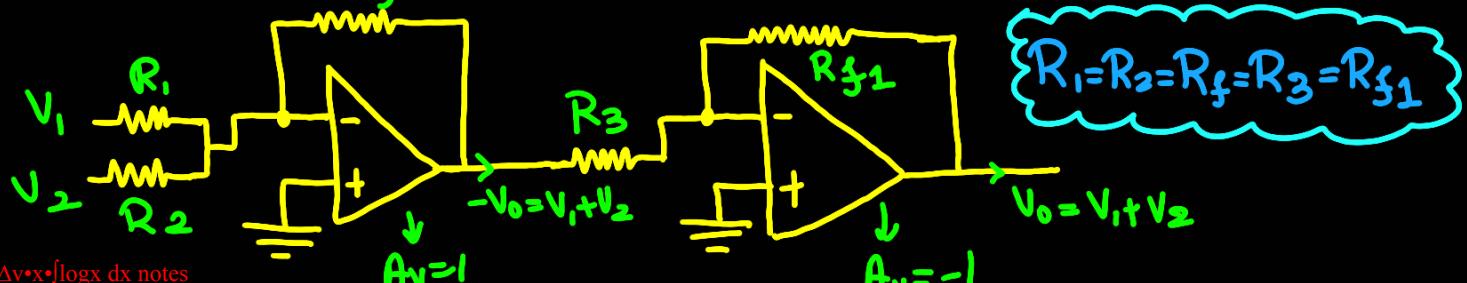

Subtractor :-

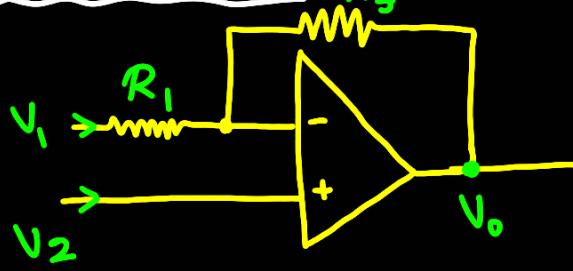

To prove :- $V_0 = V_2 - V_1$

$$V_{o1} = -\frac{R_f}{R_1} (V_1)$$


$$V_{o2} = \left(1 + \frac{R_f}{R_1}\right) (V_2)$$

Taking $R_f = R_1 = 1$ $\Rightarrow V_{o1} = -V_1$ \rightarrow We need this

$\Rightarrow V_{o2} = 2V_2$ \rightarrow We don't need this

$\frac{1}{2}$ \rightarrow Thus we need to divide!

Use a \downarrow voltage divider

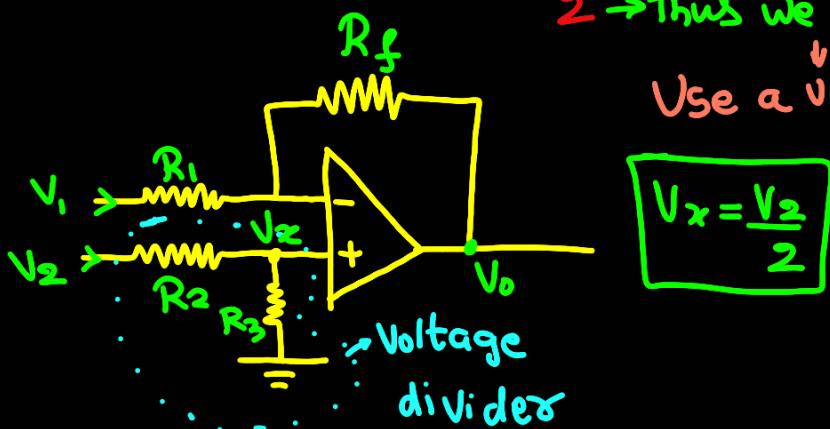

Expression for O/P voltage :-

O/P voltage due to V_1 is V_{o1} given by

$$V_{o1} = -\frac{R_f}{R_1} V_1 \rightarrow ①$$

O/P voltage due to V_2 is V_{o2} given by

$$V_{o2} = \left(1 + \frac{R_f}{R_1}\right) V_2 \rightarrow ②$$

$$V_x = R_3 \left(\frac{V_2}{R_2 + R_3}\right) \rightarrow ③$$

Thus from ③, ② now becomes

$$V_x = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3 V_2}{R_2 + R_3}\right)$$

$$V_o = V_{o1} + V_{o2}$$

$$V_o = \frac{-R_f}{R_1} V_1 + \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_2$$


Let $R_1 = R_2 = R_3 = R_f = R$

$$V_o = -\frac{R}{R} V_1 + \left(1 + \frac{R}{R}\right) \left(\frac{R}{R+R}\right) V_2 = -V_1 + V_2$$

$\therefore V_o = V_2 - V_1$ Thus it is used as a subtractor

Integrator:-

↳ Op-amp is used for integration

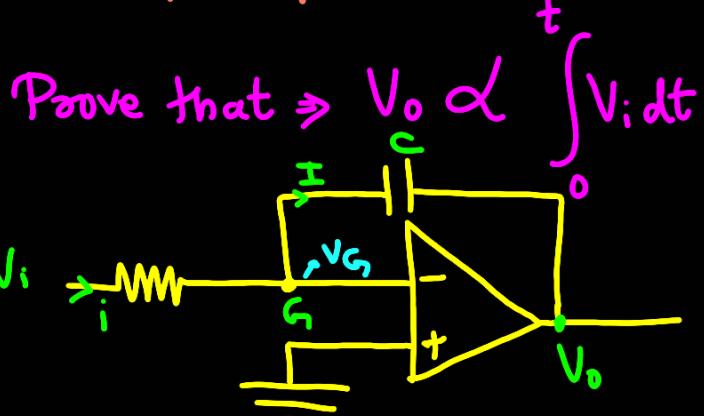

Voltage across capacitor C is $V_G - V_o = \frac{q_V}{C} \Rightarrow -V_o = \frac{q_V}{C}$ ①

$$\text{WKT} \Rightarrow q_V = \int_0^t i dt \rightarrow ②$$

From the ckt $i = \frac{V_i - V_G}{R} = \frac{V_i}{R}$ ③ ($V_G = 0$)

Put ③ & ② in ①

$$-V_o = \frac{1}{C} \int_0^t i dt = \frac{1}{C} \int_0^t \frac{V_i}{R} dt$$


$$V_o = -\frac{1}{RC} \int_0^t V_i dt$$

$\Rightarrow V_o \propto \int_0^t V_i dt$

Thus, it can be used as integrator

Differentiator :-

Op-Amp
used for
differentiation

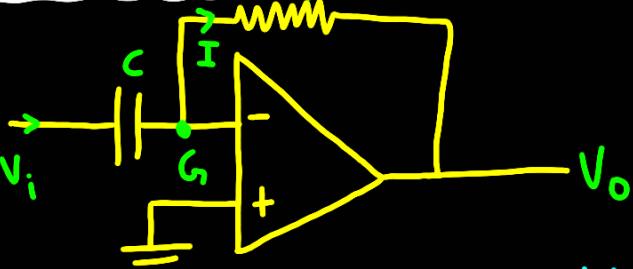

$$I = \frac{V_G - V_o}{R} = -\frac{V_o}{R} \rightarrow \textcircled{1}$$

$$V_i - V_G = \frac{q}{C} \Rightarrow q = CV_i \rightarrow \textcircled{2}$$

$$\frac{1}{V_G} = 0$$

Differentiating $\textcircled{2}$, we get

$$\frac{dq}{dt} = C \frac{dV_i}{dt} \Rightarrow -\frac{V_o}{R} = C \frac{dV_i}{dt}$$


$$-V_o = RC \frac{dV_i}{dt}$$

$$V_o = -RC \frac{dV_i}{dt} \Rightarrow V_o \propto \frac{dV_i}{dt}$$

Thus it can be used as differentiator

Comparator :-

* Compare V_2 with V_1

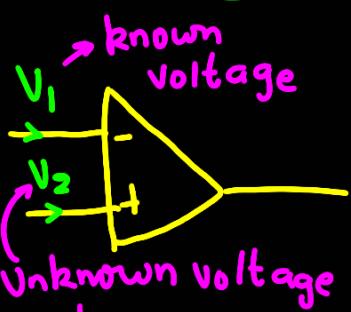


- * $V_2 < V_1 \Rightarrow$ O/P is -Ve
- * $V_2 = V_1 \Rightarrow$ O/P is Zero
- * $V_2 > V_1 \Rightarrow$ O/P is +Ve

Oscillators using OP Amps


* We do not know how to design amplifiers using BJT yet
but we do know how to make one using Op-Amps

Consider the following:-

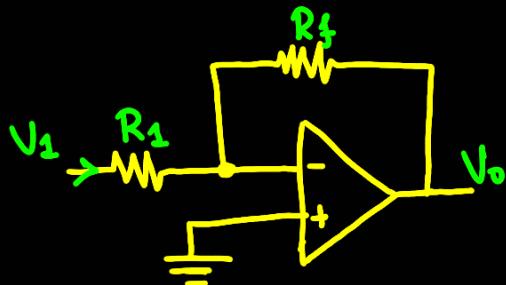

Inverting Amplifier
↓
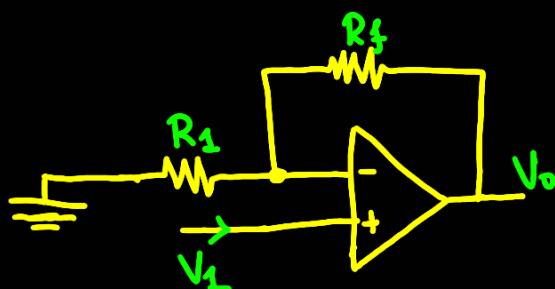
$$\text{Amplifier Gain} = -\frac{R_f}{R_1}$$




Non-inverting Amplifier
↓

$$\text{Amplifier Gain} = 1 + \frac{R_f}{R_1}$$

Example question:- Design Crystal oscillator using Op-Amp
We can use either of the 2 Op-Amp amplifiers

Inverting amplifier

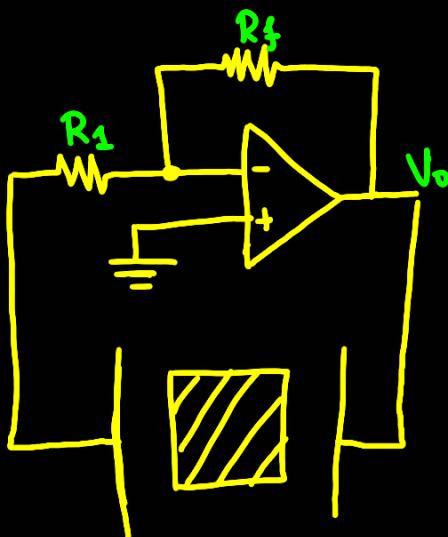

$$\text{WKT, Gain of Crystal} = \frac{1}{2q} = B$$


To satisfy Barkhausen Criteria

Amplifier Gain must be $2q$.. let $R_f = 29k\Omega$

$$\therefore A = -\frac{R_f}{R_1} = -\frac{29}{1} \quad \text{--- v/e}$$

$$R_1 = 1k\Omega$$

Non-inverting amplifier

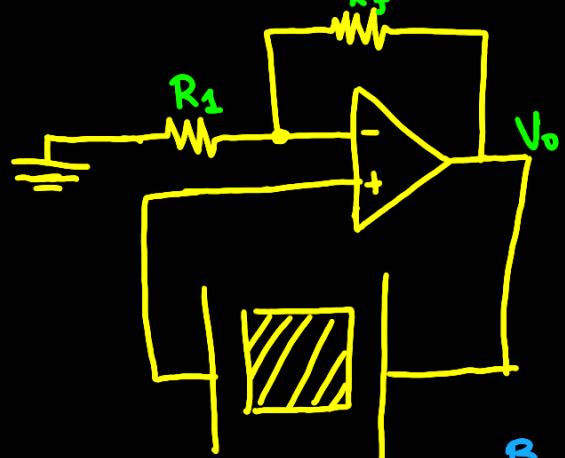

$$\text{WKT, Gain of Crystal} = \frac{1}{2q} = B$$

To satisfy Barkhausen Criteria

Amplifier Gain must be $2q \cdot R_f = 28k\Omega$

$$R_1 = 1k\Omega$$

$$\therefore A = 1 + \frac{R_f}{R_1} = 1 + \frac{28}{1} = \underline{\underline{29}} \rightarrow \text{v/e answer}$$

MORE feasible

thus we need to have another Op-Amp for v/e answer → NOT feasible